


Design IV

E232 Fall 07


Class 3

Bruce McNair
bmcnair@stevens.edu

Measurement Systems

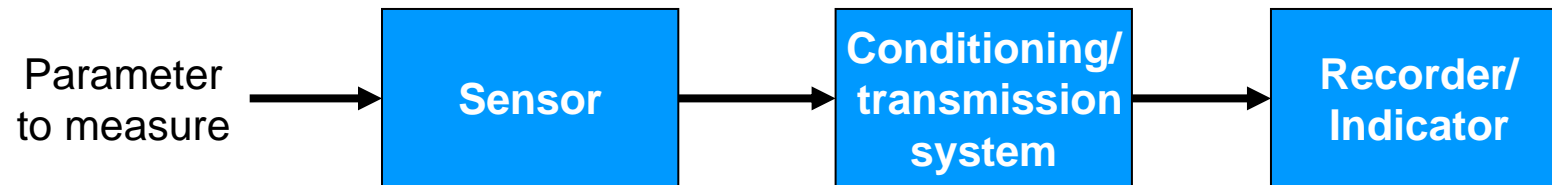


Measurement Systems

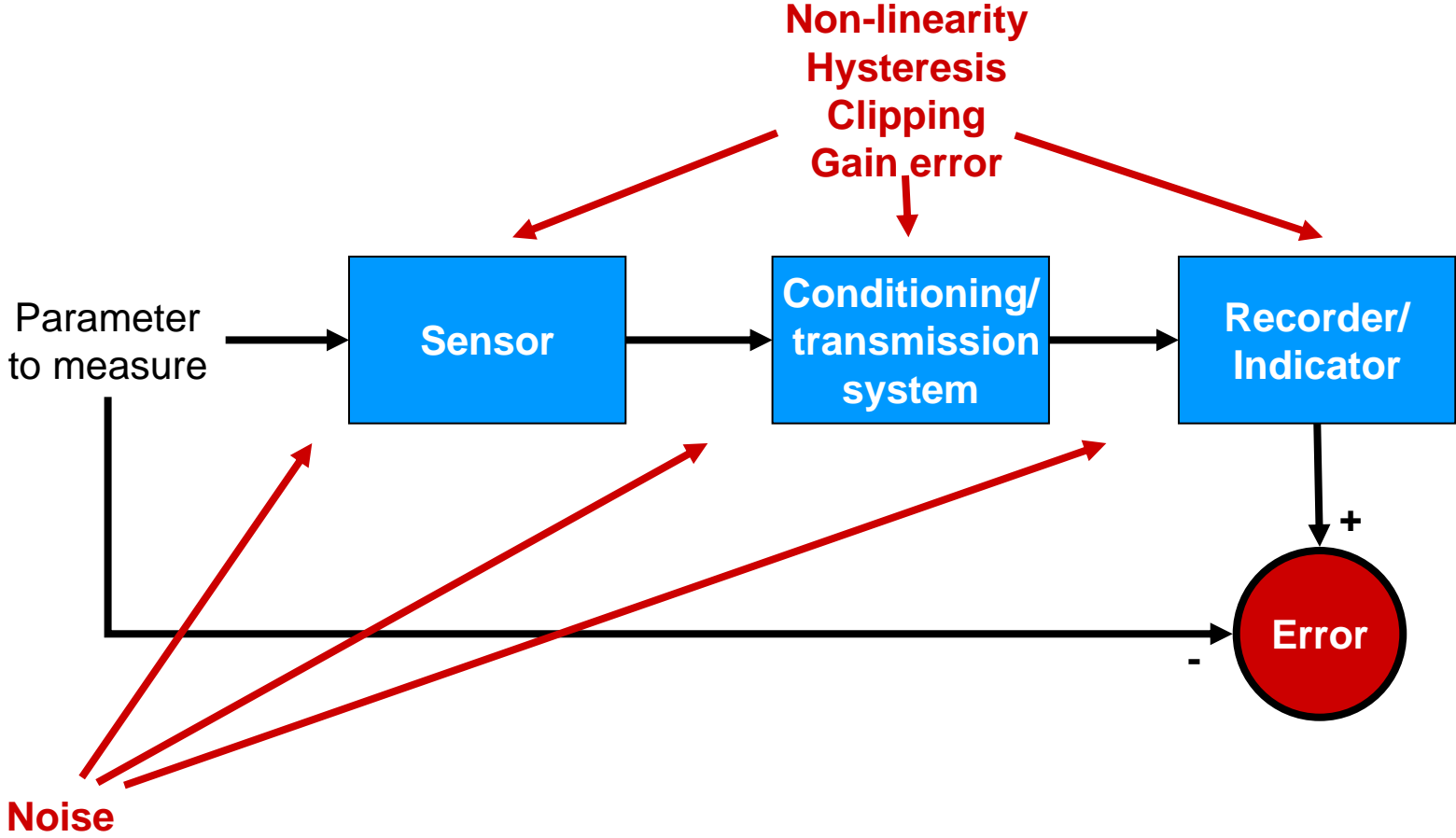


Dynamic Systems

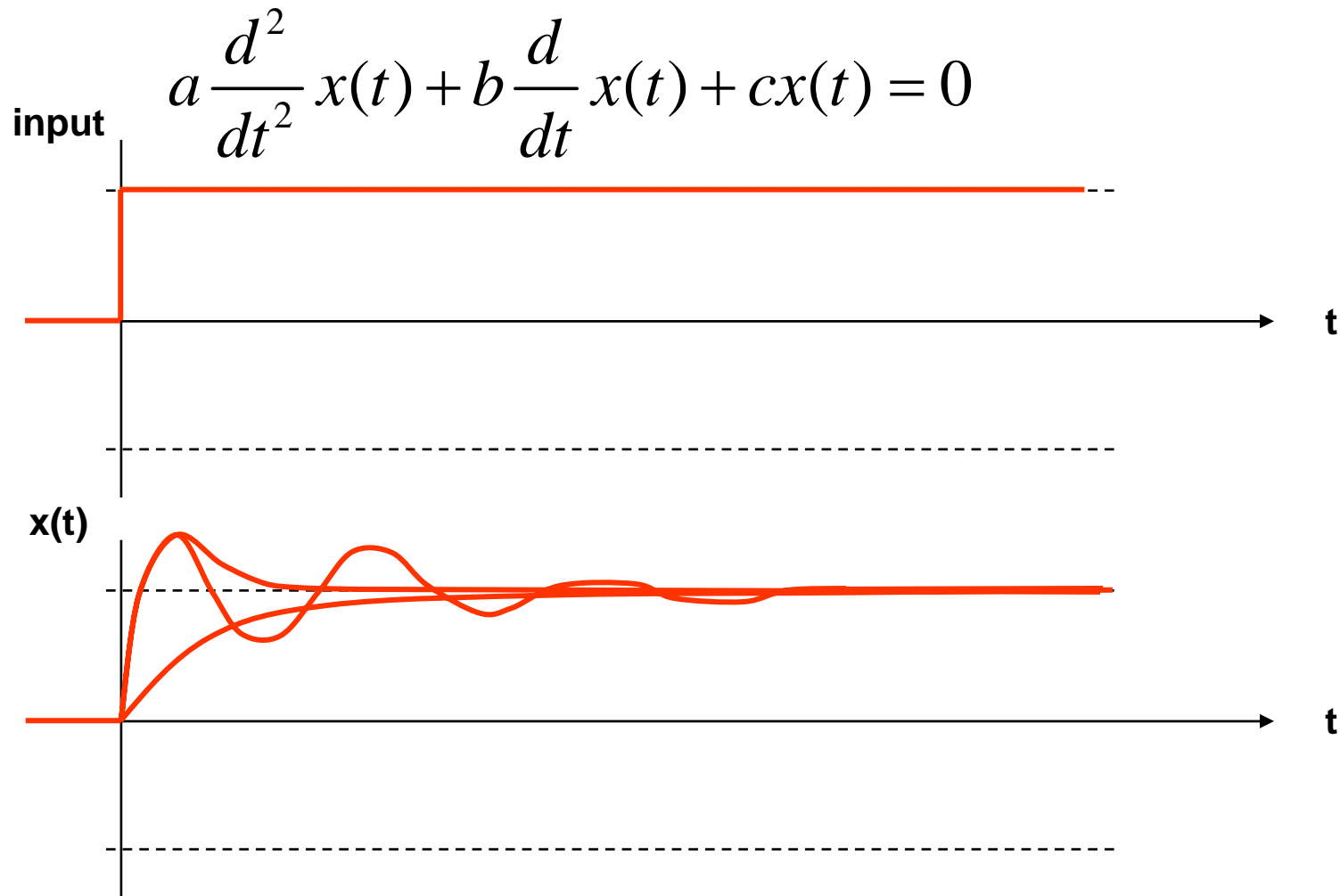- Second-order system performance measures



Frequency Response

- Practical low-pass response

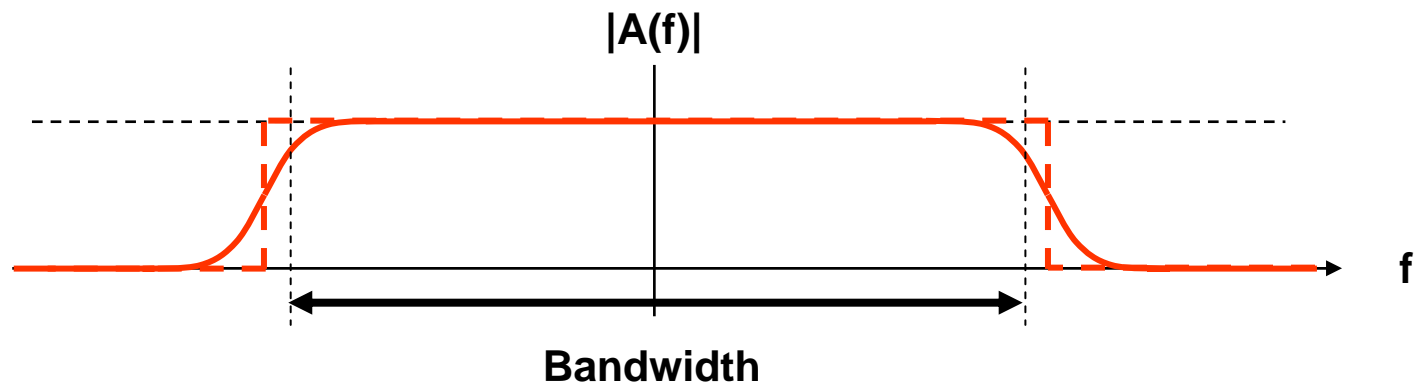


Today's topics

- Why deal with electrical signals?
- Signal conditioning, transformation
 - Amplifiers
 - Gain
 - Bandwidth
 - Phase shift
 - Common mode rejection


Electrical Signals In a Physical World

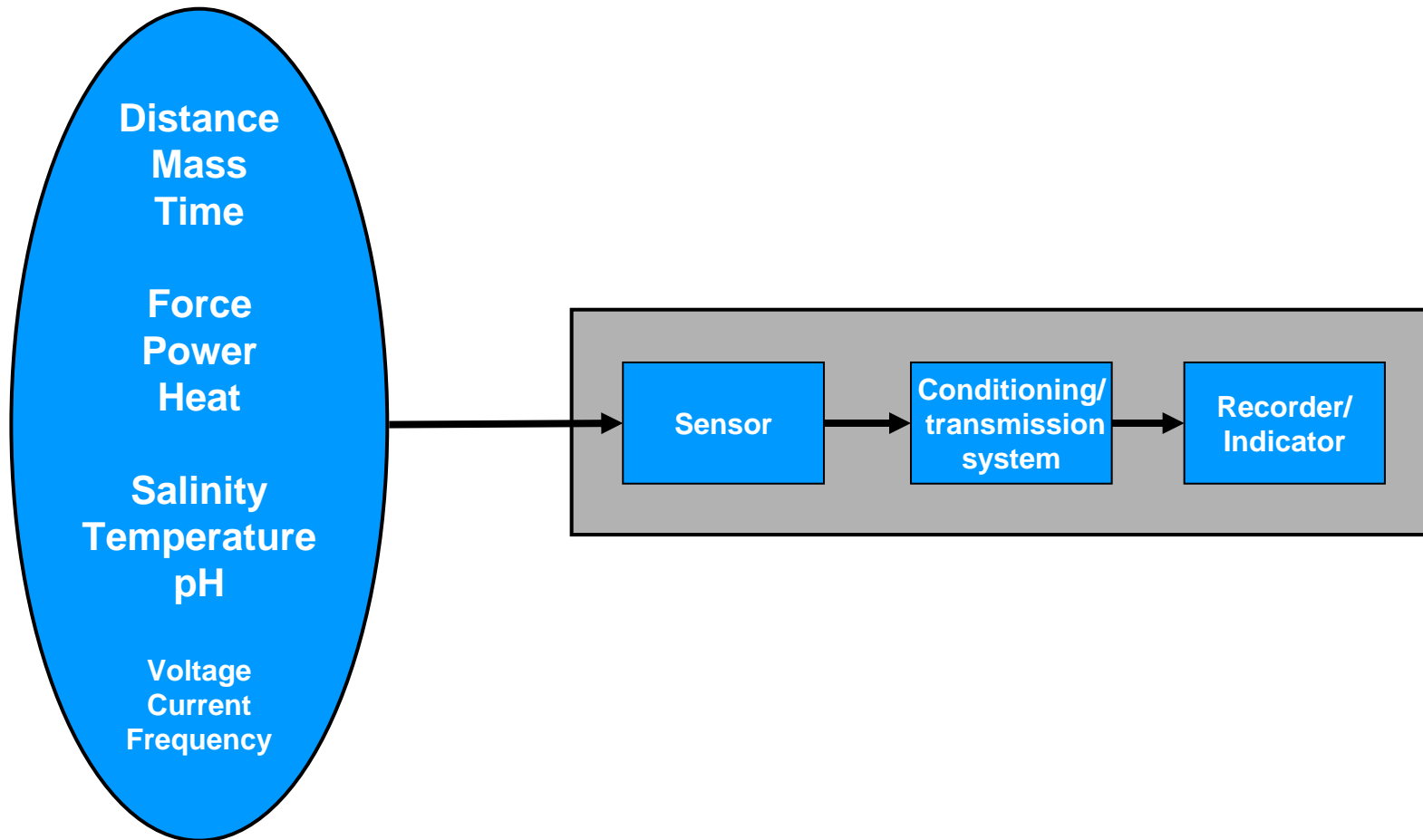- Most parameters we want to sense and record have physical values




Electrical Signals In a Physical World

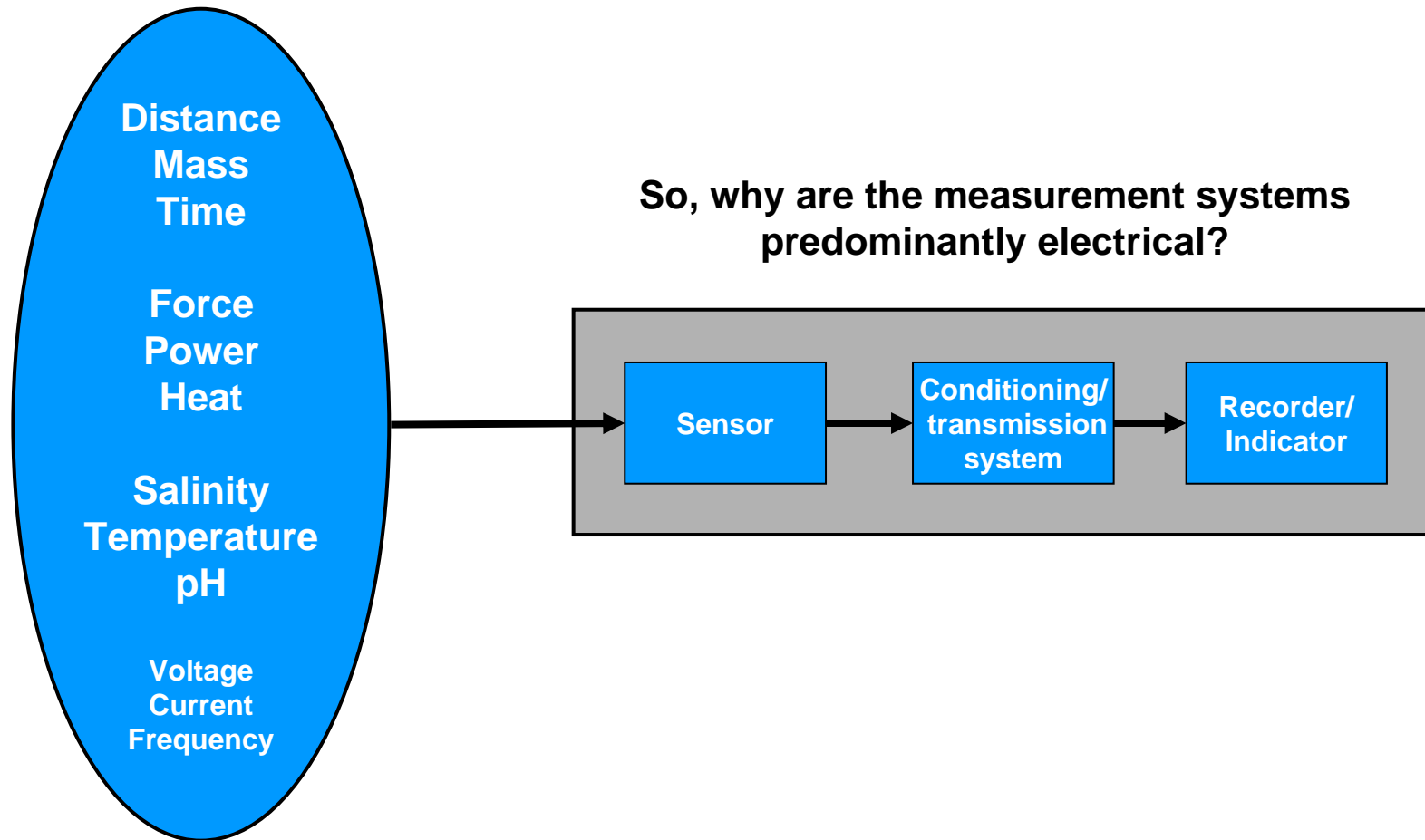- Most parameters we want to sense and record have physical values



Electrical Signals In a Physical World

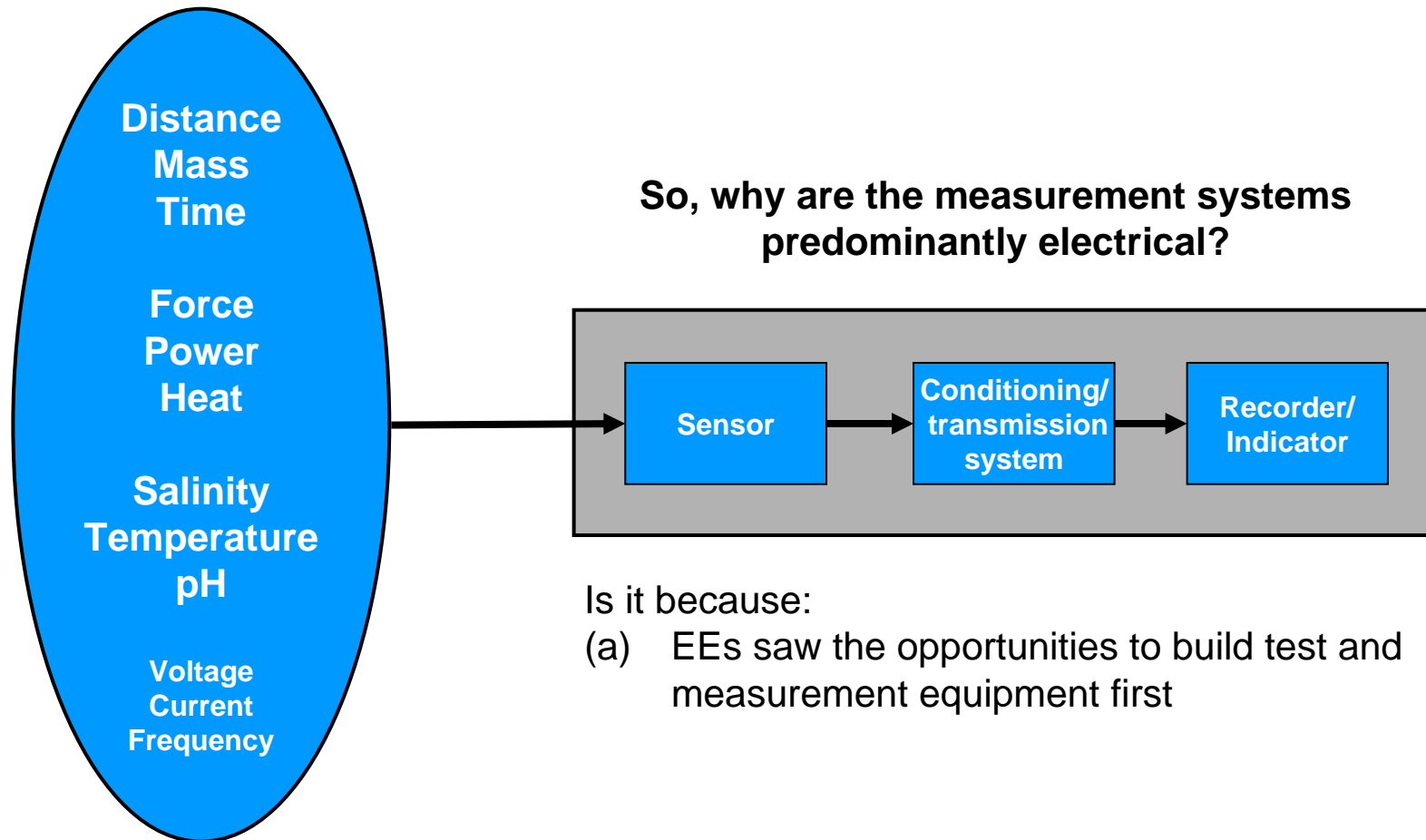- Most parameters we want to sense and record have physical values




Is it because:

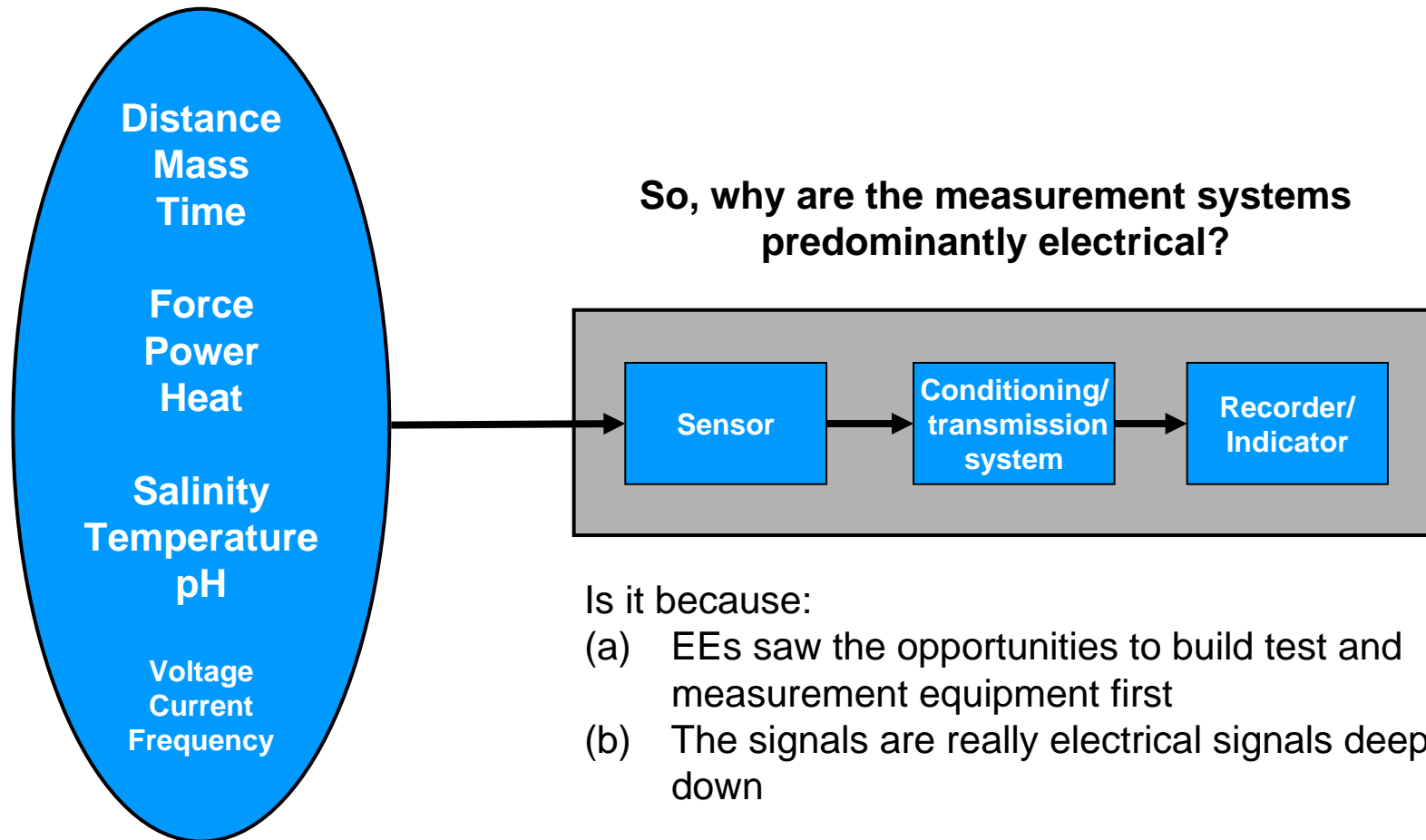- (a) EEs saw the opportunities to build test and measurement equipment first

Electrical Signals In a Physical World

- Most parameters we want to sense and record have physical values




Is it because:

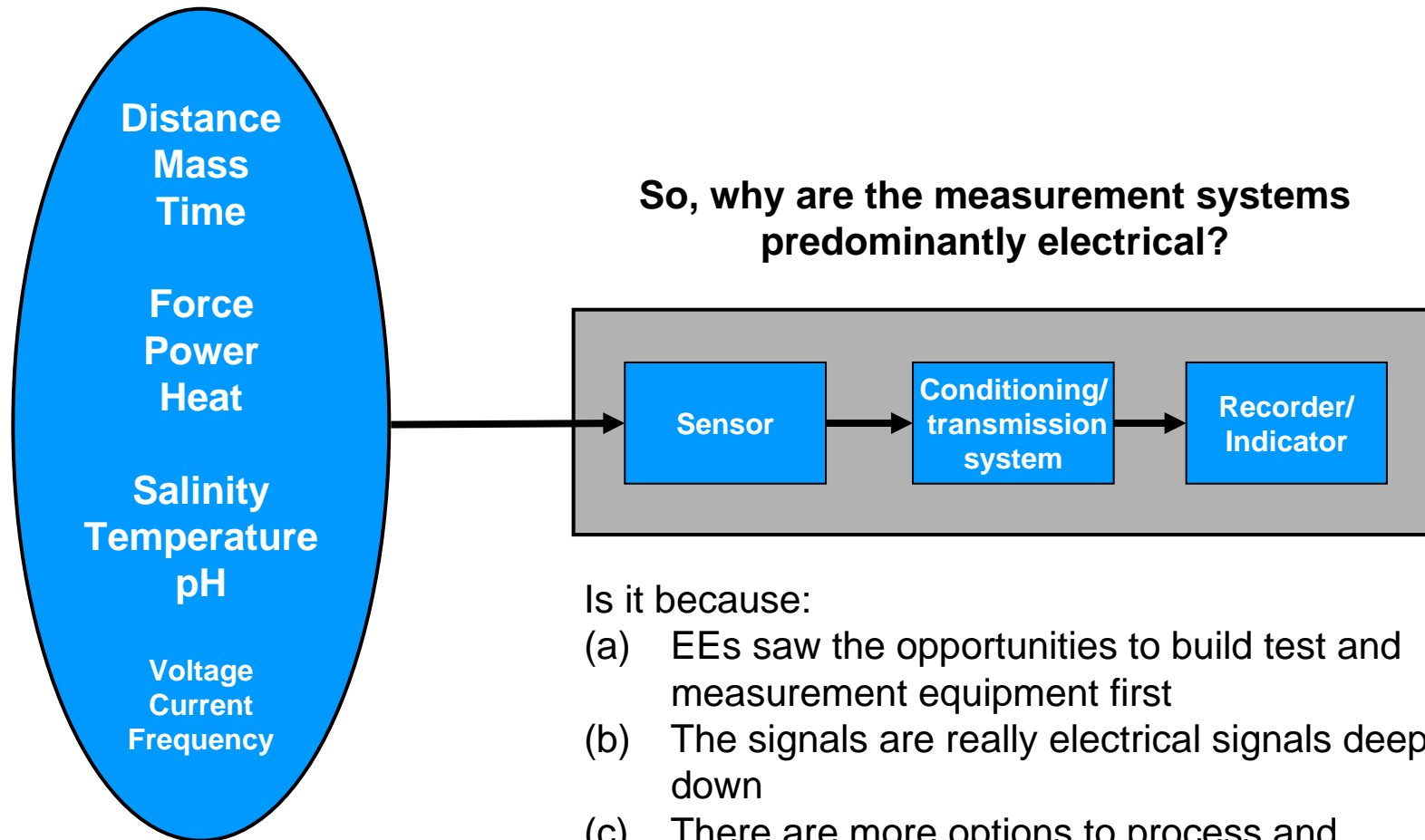- (a) EEs saw the opportunities to build test and measurement equipment first
- (b) The signals are really electrical signals deep down

Electrical Signals In a Physical World

- Most parameters we want to sense and record have physical values




Is it because:

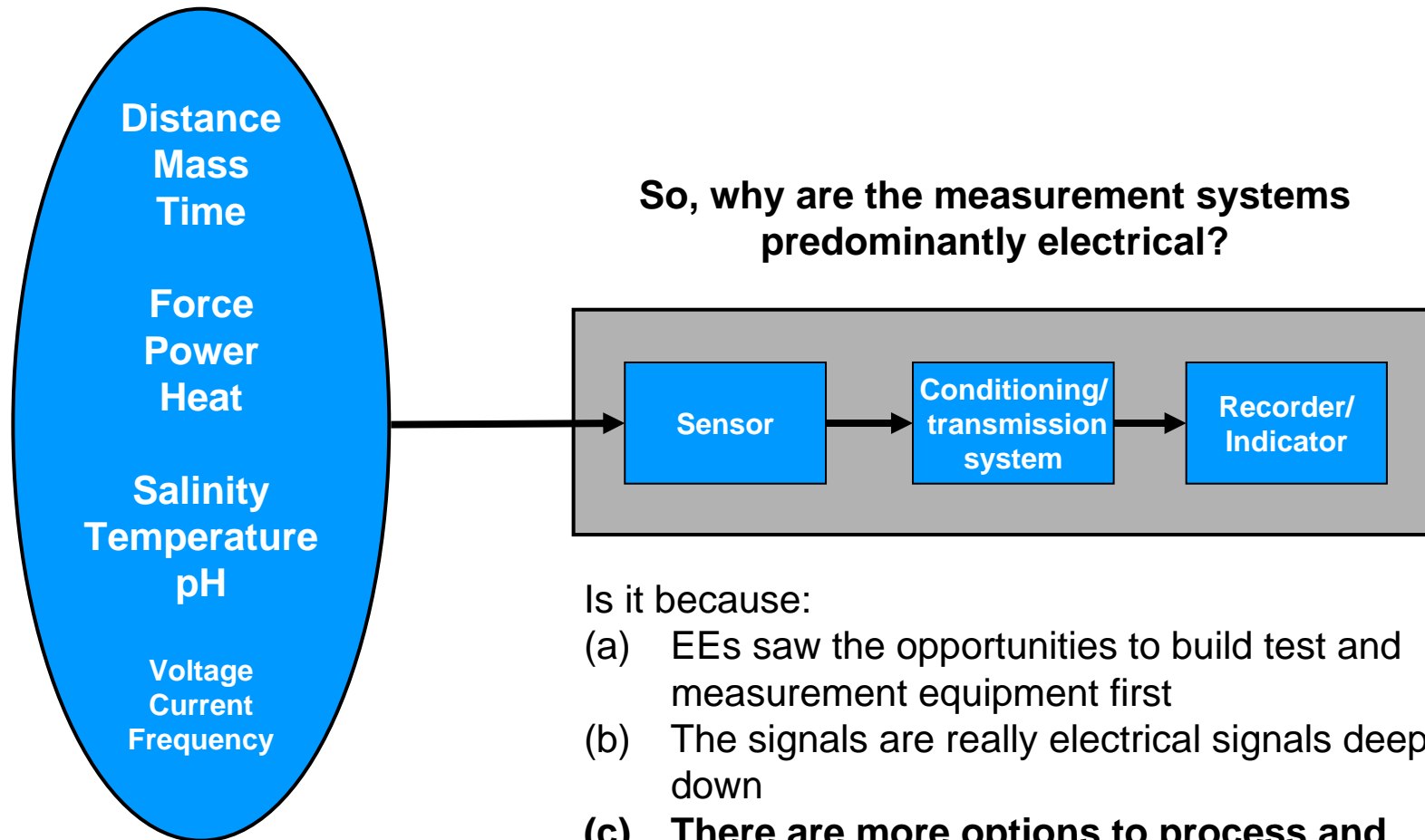- (a) EEs saw the opportunities to build test and measurement equipment first
- (b) The signals are really electrical signals deep down
- (c) There are more options to process and transmit signals in electrical form

Electrical Signals In a Physical World


- Most parameters we want to sense and record have physical values



Is it because:


- (a) EEs saw the opportunities to build test and measurement equipment first
- (b) The signals are really electrical signals deep down
- (c) There are more options to process and transmit signals in electrical form**

Signal Conditioning And Transformation

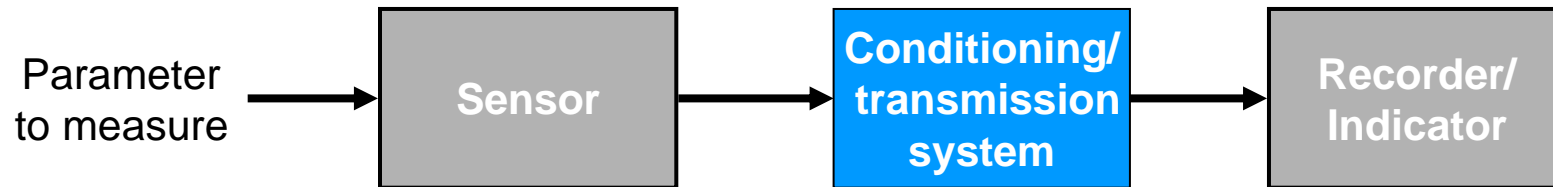


Signal Conditioning And Transformation

- Amplification

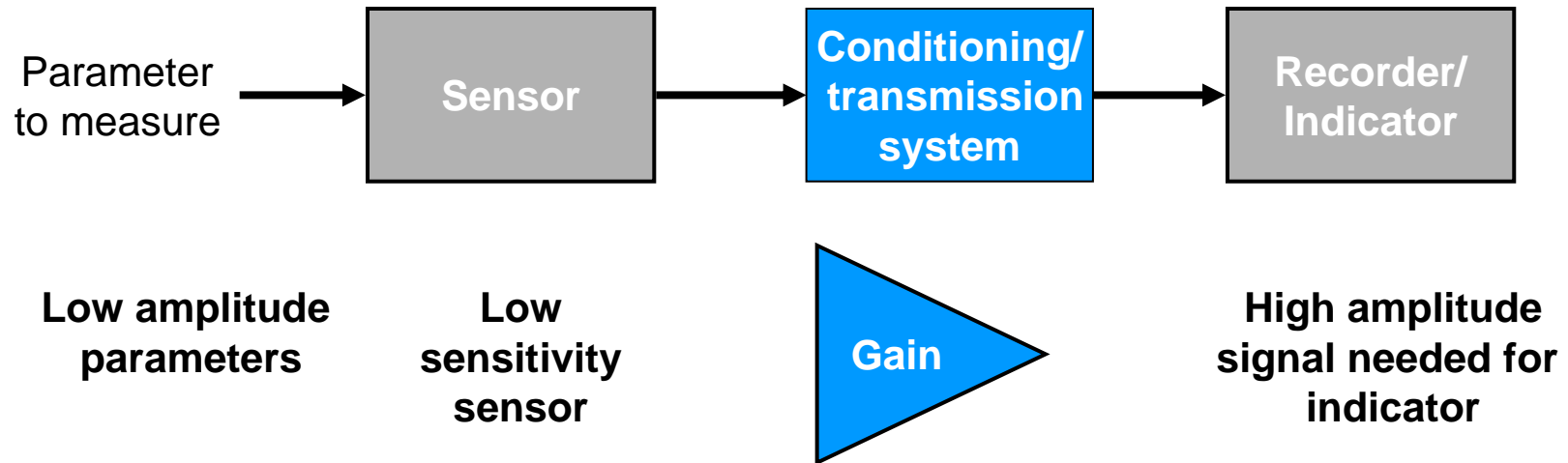

Signal Conditioning And Transformation


- Amplification

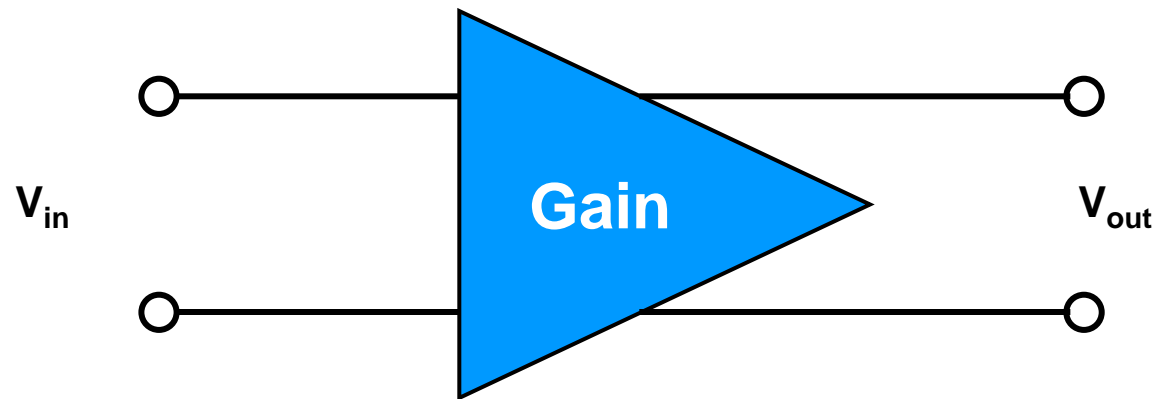

$$G = \frac{V_{out}}{V_{in}}$$

Signal Conditioning And Transformation


- Amplification

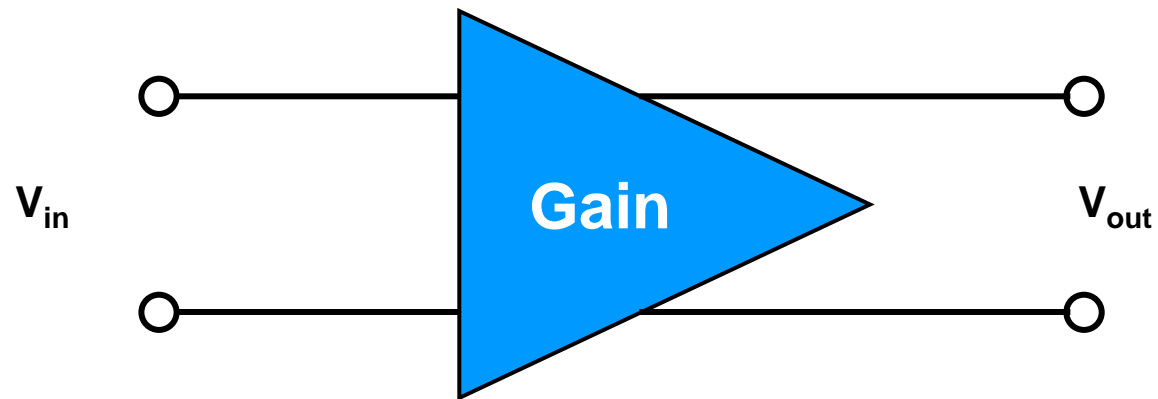

$$G_{dB} = 20 \cdot \log_{10} \left(\frac{V_{out}}{V_{in}} \right)$$

Signal Conditioning And Transformation

- Amplification

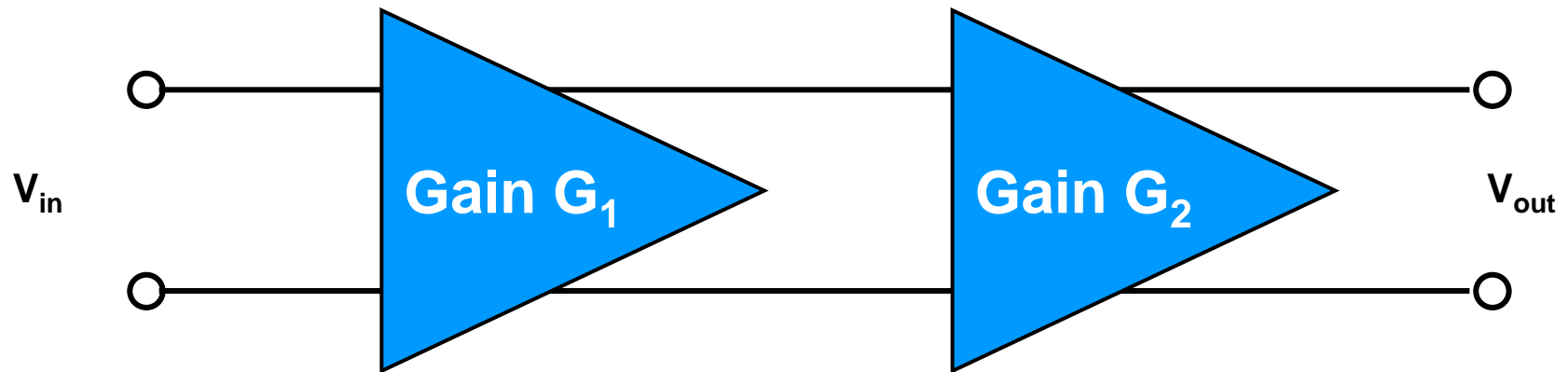


$$G_{overall} = G_1 \cdot G_2$$

$$G_{overall_{dB}} = G_{1_{dB}} + G_{2_{dB}}$$

Signal Conditioning And Transformation


- Amplification

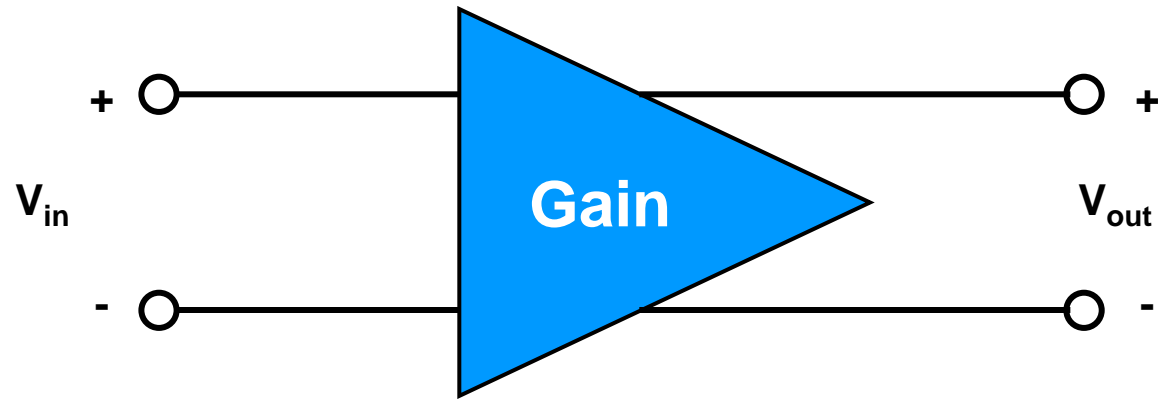

Balanced inputs/outputs

Signal Conditioning And Transformation


- Amplification

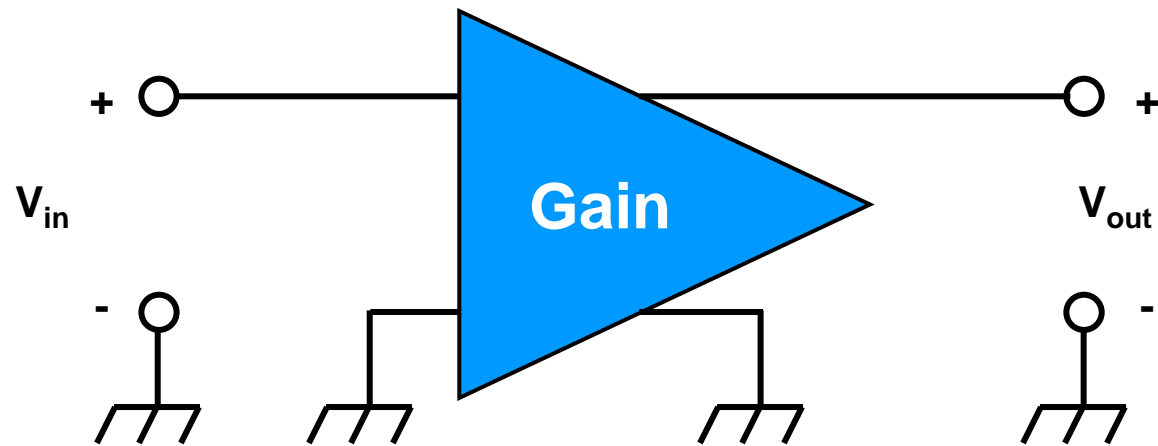

Unbalanced (single-ended) inputs/outputs

Signal Conditioning And Transformation

- Attenuation

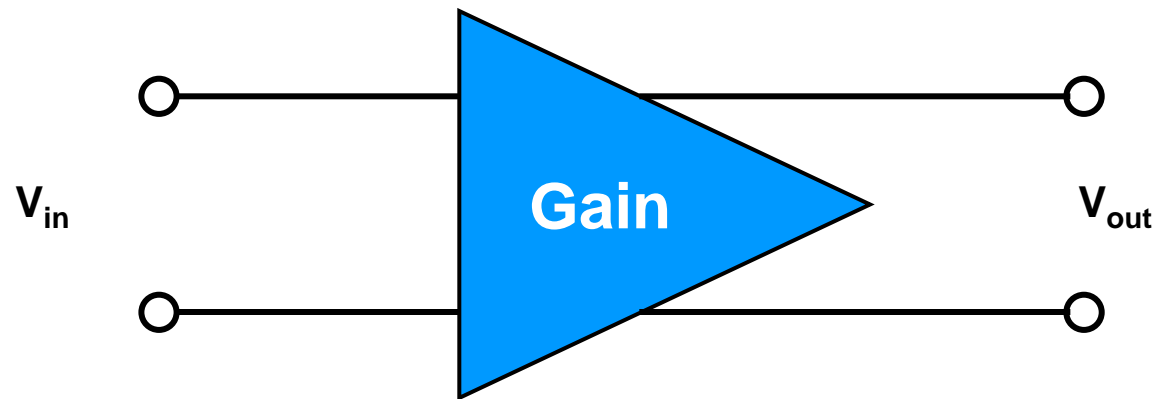


$$G < 1$$

$$G_{dB} < 0$$

Signal Conditioning And Transformation


- Amplifier characteristics

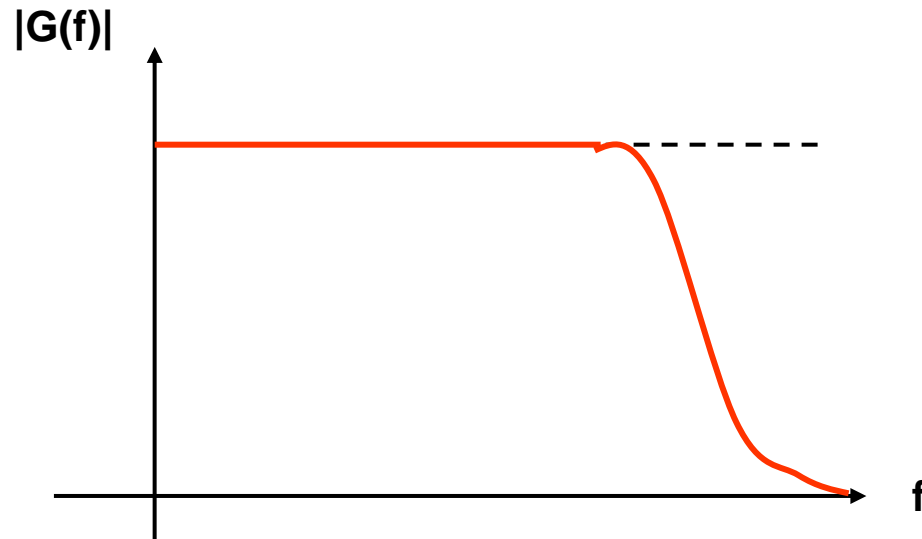

Lowpass frequency response


Signal Conditioning And Transformation

- Amplifier characteristics

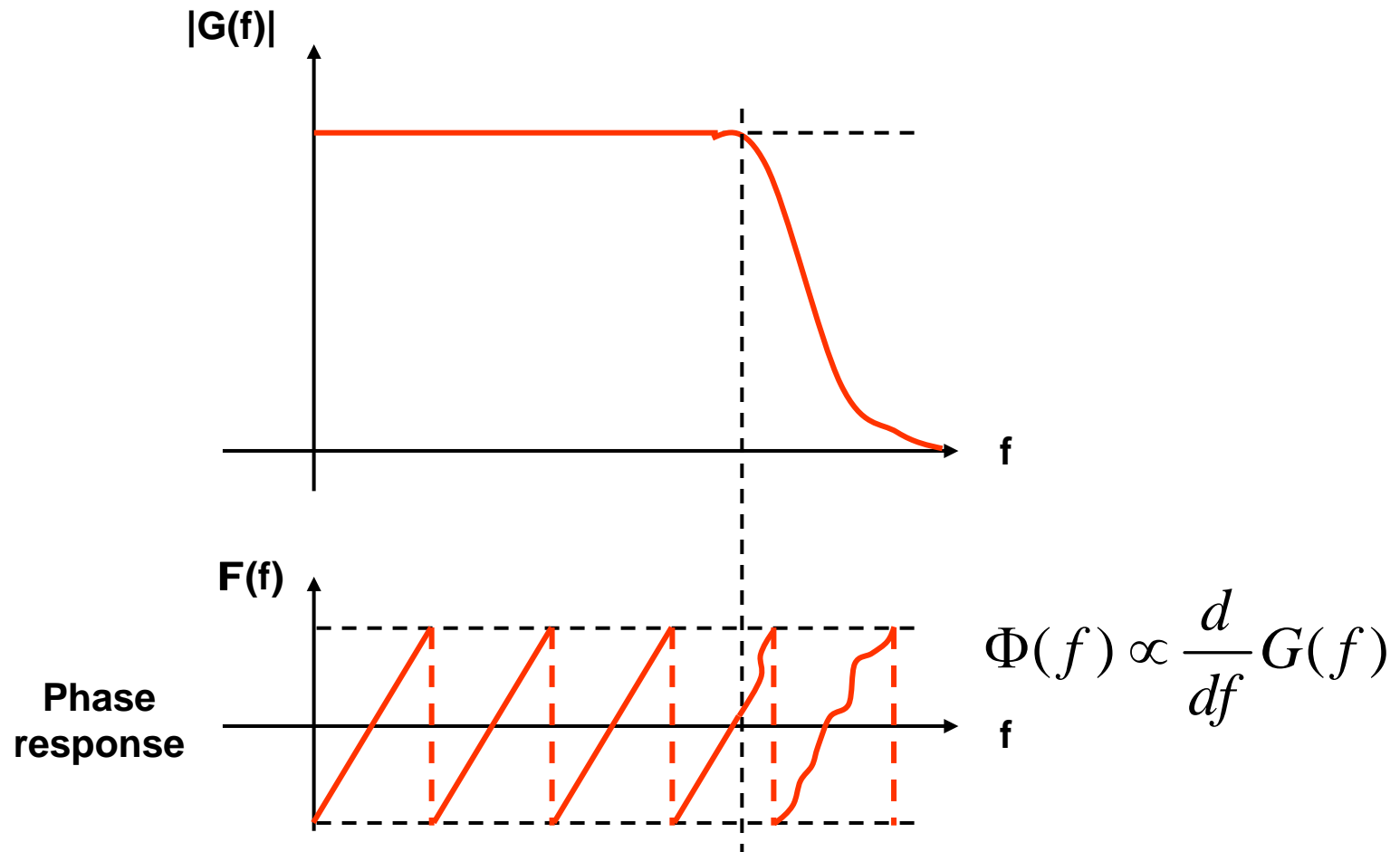


Signal Conditioning And Transformation

- Amplifier characteristics

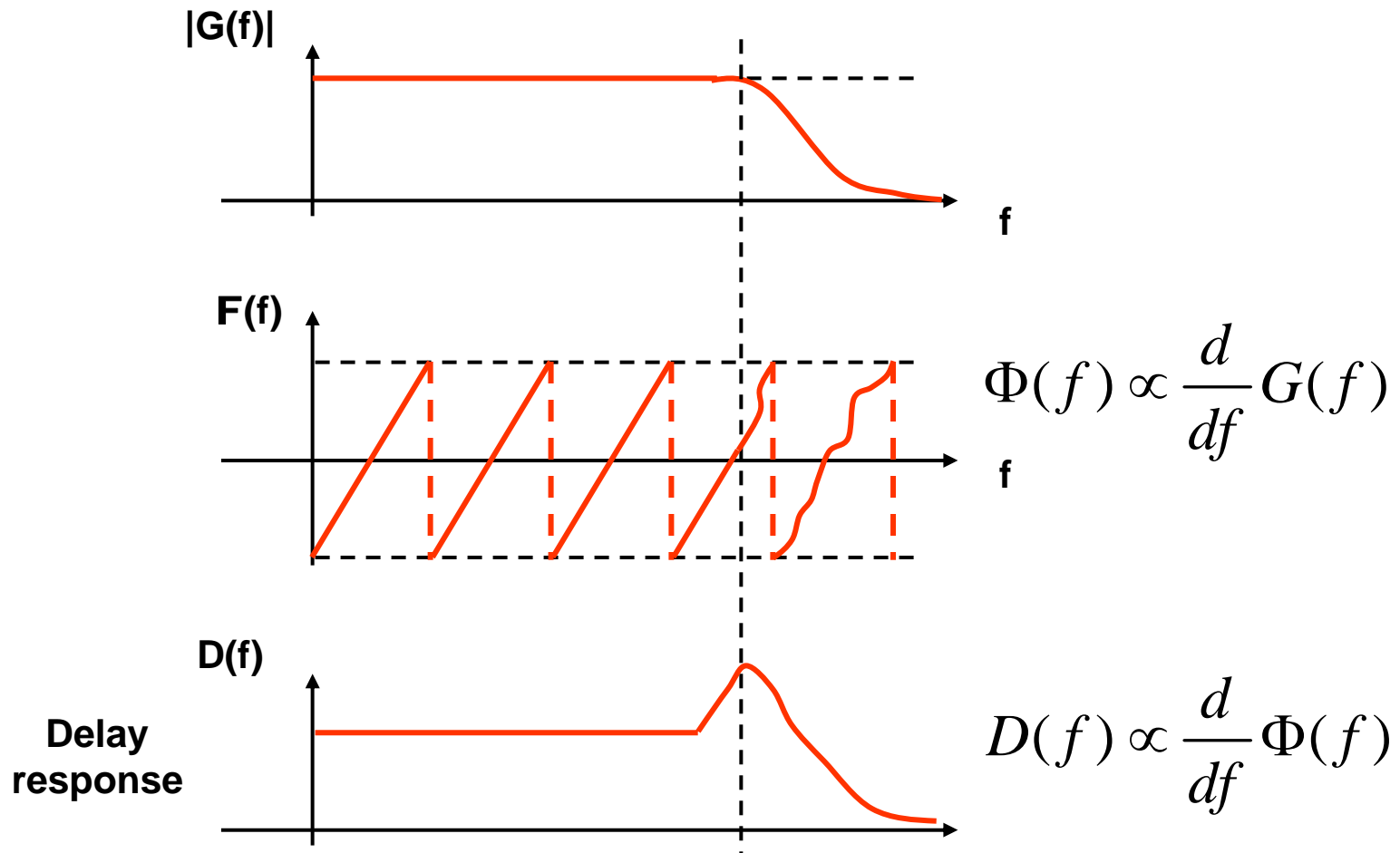


Effect Of Phase-Shift Variation

- Sinusoidal signals:

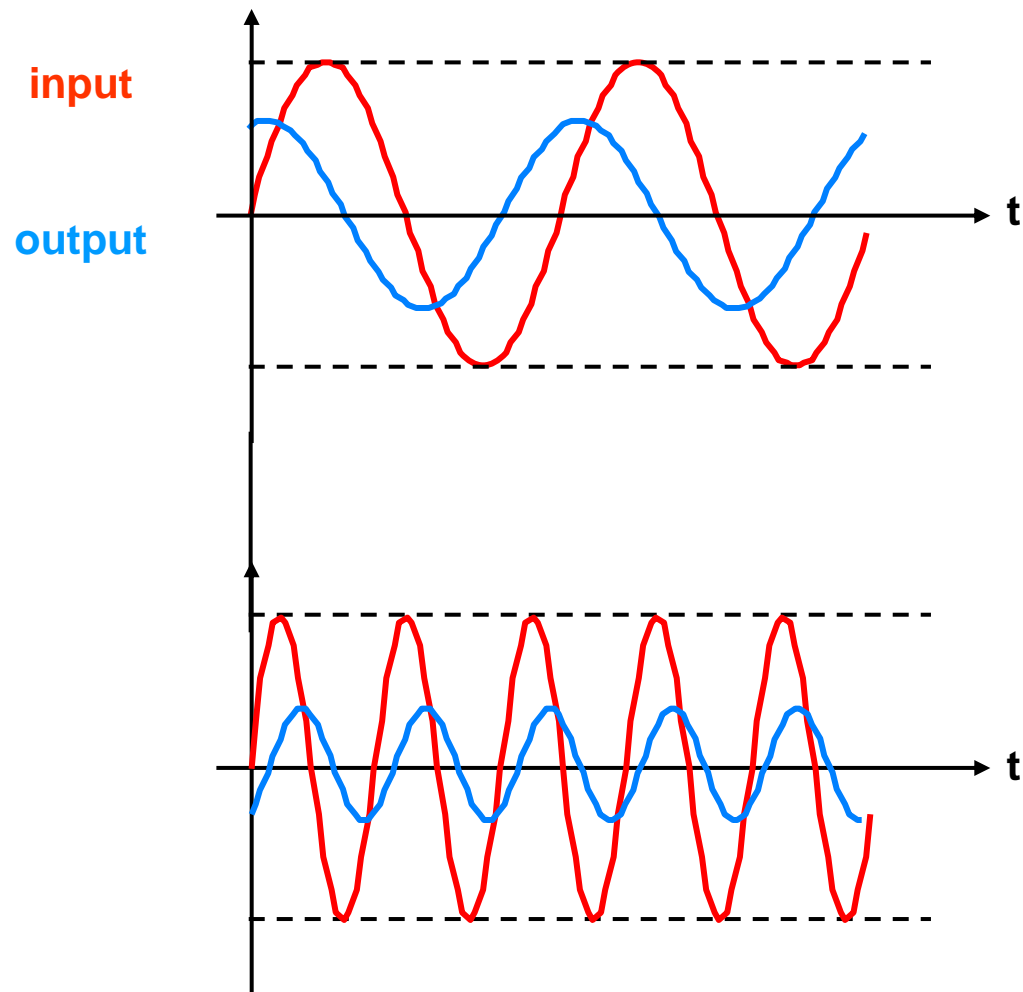

Effect Of Phase-Shift Variation


- Non-sinusoidal signals:

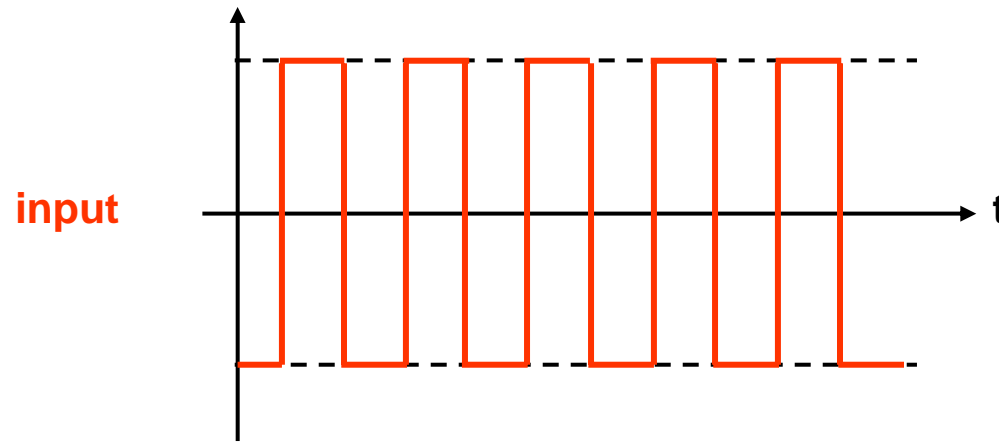


$$\sum_{i=1}^{\infty} \frac{\sin((2 \cdot i + 1) \cdot 2\pi f t)}{2 \cdot i + 1}$$

Effect Of Phase-Shift Variation

- Non-sinusoidal signals:

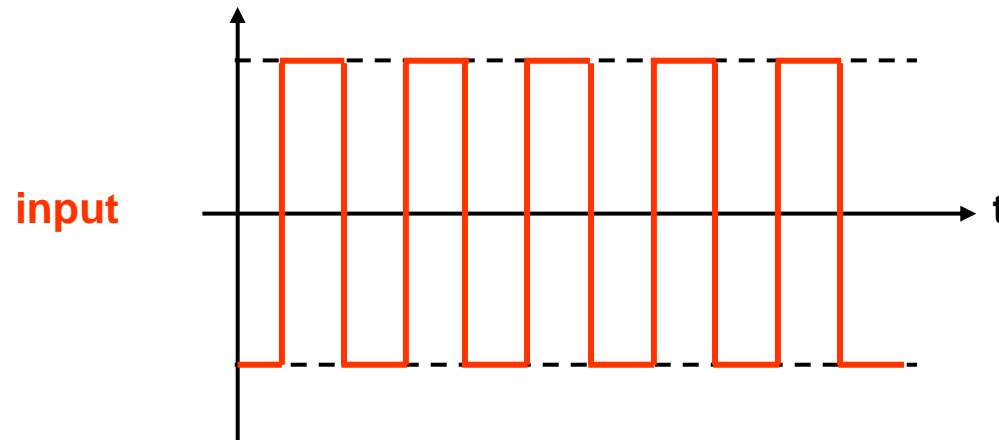

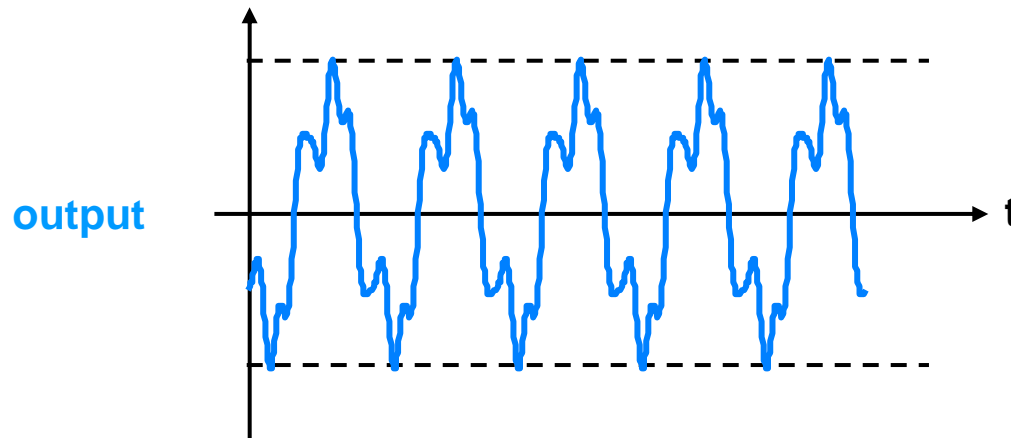
$$\sum_{i=1}^{\infty} \frac{\sin((2 \cdot i + 1) \cdot 2\pi f t)}{2 \cdot i + 1}$$



Signal Conditioning And Transformation

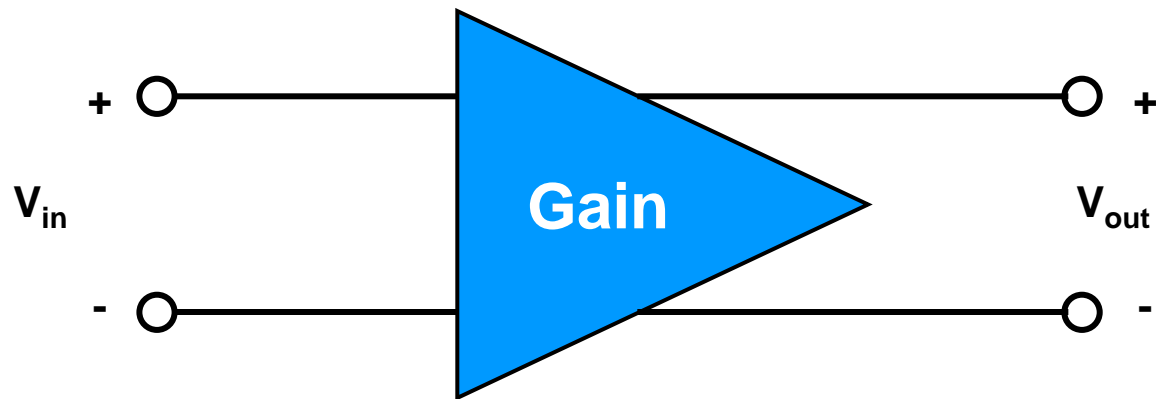- Other amplifier impairments – Common Mode Rejection Ratio




Ideally:

$$V_{out} = G \cdot (V_{in}^{+} - V_{in}^{-})$$

Signal Conditioning And Transformation

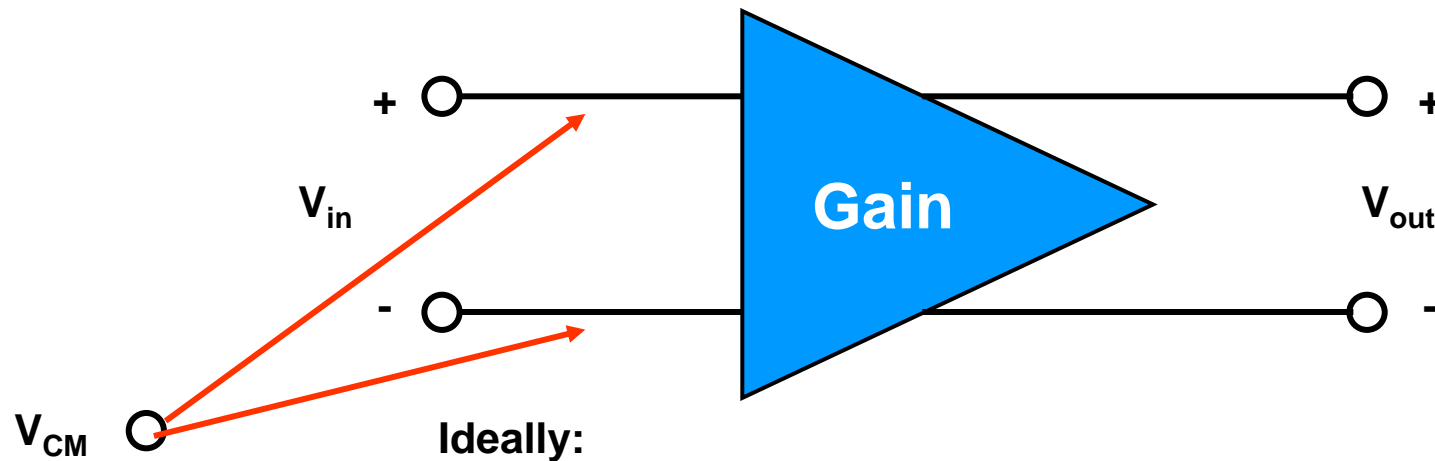- Other amplifier impairments – Common Mode Rejection Ratio



Ideally:


$$V_{out} = G \cdot (V_{in}^+ - V_{in}^-)$$

Practically:

$$V_{out} = G_{diff} \cdot (V_{in}^+ - V_{in}^-) + G_{CM} \cdot (V_{CM})$$

Signal Conditioning And Transformation

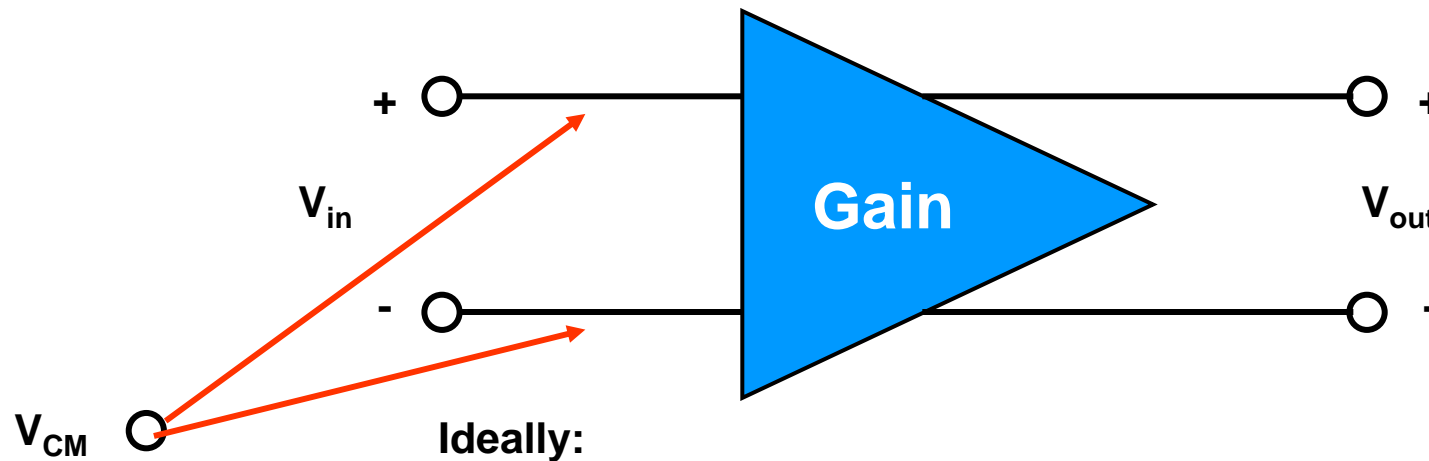- Other amplifier impairments – Common Mode Rejection Ratio



Ideally:

$$V_{out} = G \cdot (V_{in}^+ - V_{in}^-)$$


Practically:

$$V_{out} = G_{diff} \cdot (V_{in}^+ - V_{in}^-) + G_{CM} \cdot (V_{CM})$$

$$CMRR = 20 \cdot \log \left(\frac{G_{diff}}{G_{CM}} \right)$$


Signal Conditioning And Transformation

- Amplifier impedance

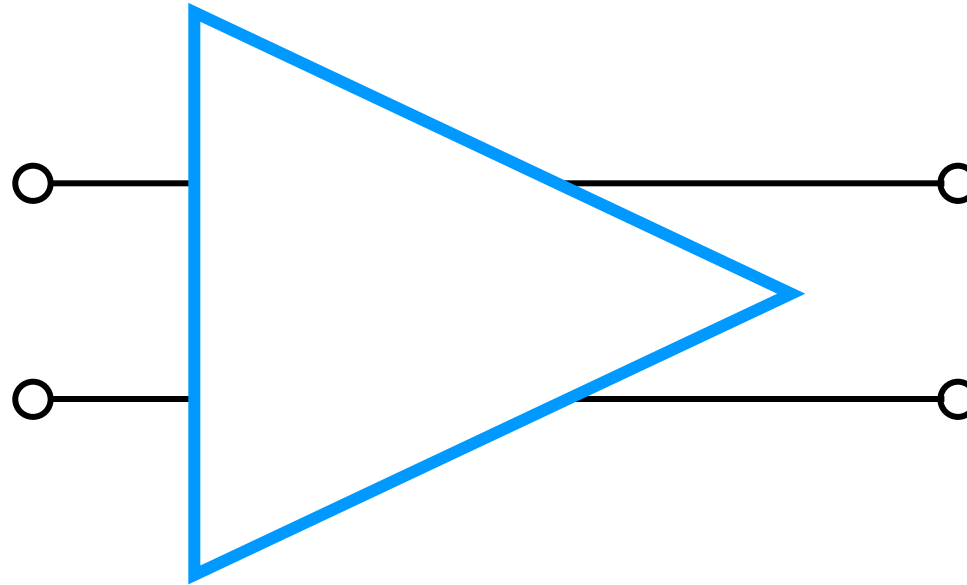


Signal Conditioning And Transformation

- Amplifier impedance

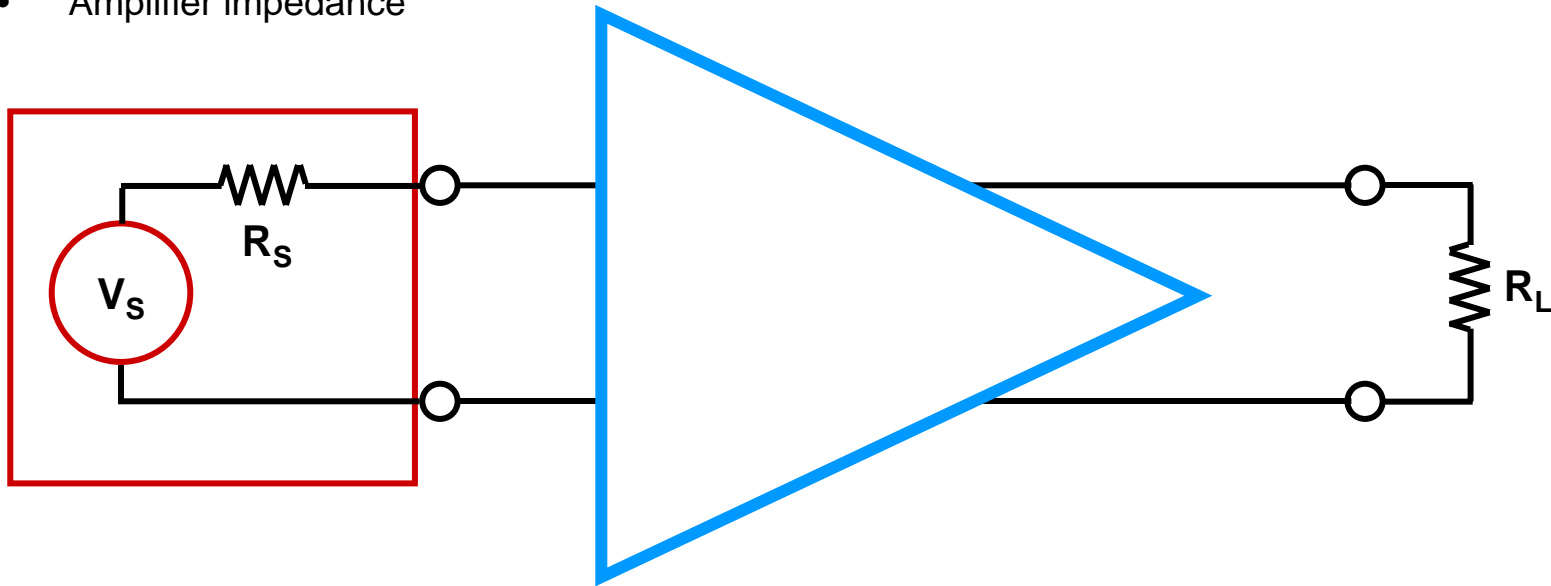

Signal Conditioning And Transformation

- Amplifier impedance

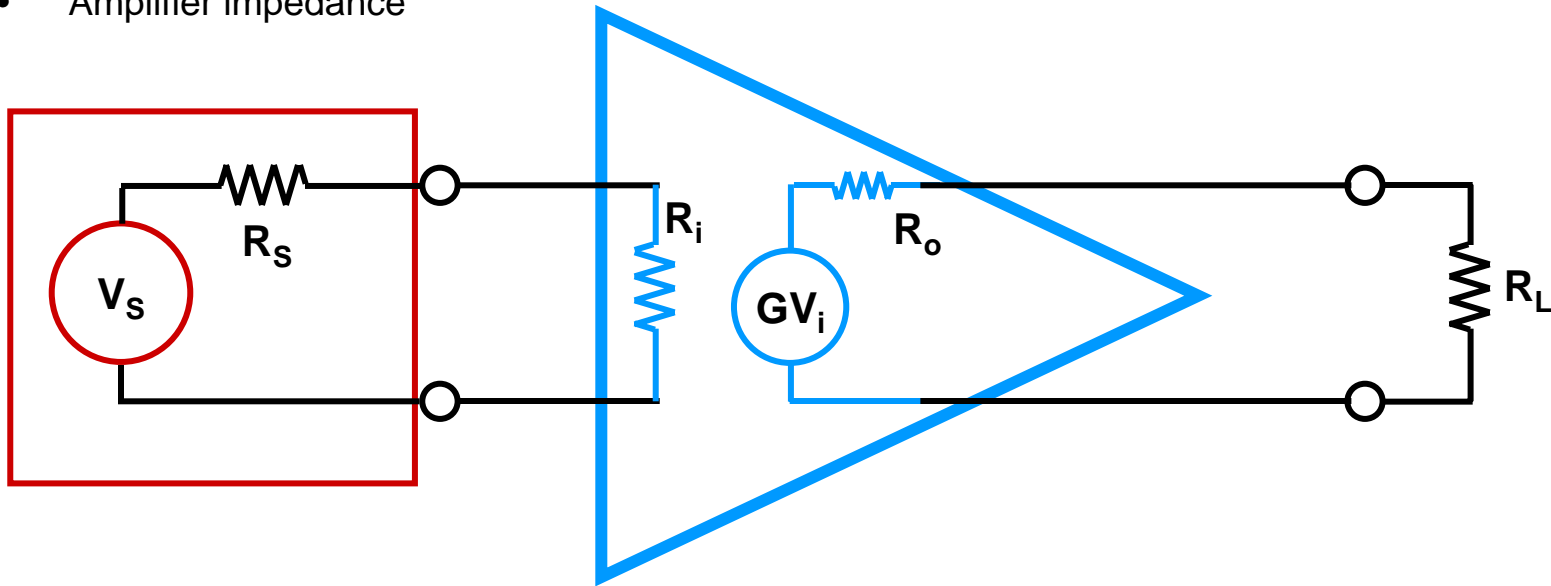

For greatest voltage gain, best frequency response:

$$R_i \rightarrow \infty$$

$$R_o \rightarrow 0$$

Next topics

- Signal conditioning, transformation
 - Amplifiers
 - DC drift
 - Operational Amplifiers
 - Filtering
 - Filter families
 - Integration, differentiation, comparison
- Indicators and recording devices
 - Voltage
 - Waveforms
 - Frequency
 - Spectrum
- Transmission
 - Signal level considerations
 - Interference sources
 - Ground loops
 - Rationale for digital signal transmission