

Electronic Circuits – EE359A

Bruce McNair

B206

bmcnair@stevens.edu

201-216-5549

Filters and Tuned Amplifiers

Second order LCR resonator

Second order Active Filters based on
Inductor Replacement

Signal Generators

Oscillators

Second Order LCR Resonator

- LCR Resonator

$$\frac{V_0}{I} = \frac{1}{Y} = \frac{1}{1/sL + sC + 1/R}$$


$$= \frac{s/C}{s^2 + s(1/CR) + 1/LC}$$

$$\omega_0^2 = 1/LC$$

$$\omega_0/Q = 1/CR$$

$$\omega_0 = 1/\sqrt{LC}$$


$$Q = \omega_0 CR$$

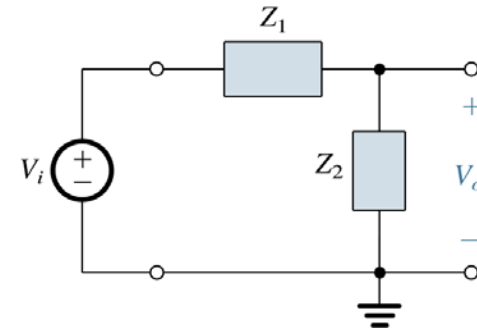

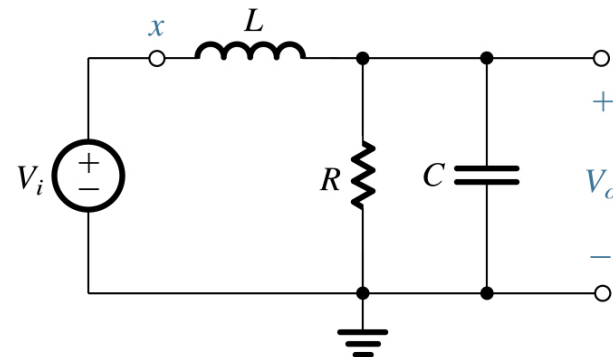(a) General structure

- Excite parallel LCR resonator

- Determine natural modes (I.e. poles of response function)




(b) LP

Transmission Zeros LPF

- Where to inject input signal V_i ?

$$T(s) = \frac{V_o(s)}{V_i(s)} = \frac{Z_2(s)}{Z_1(s) + Z_2(s)}$$

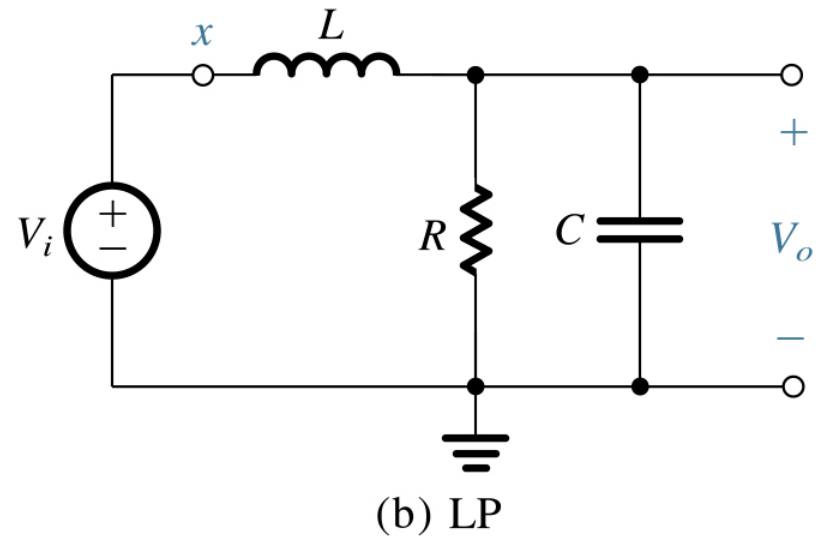- Transmission zeros are when $Z_2(s)$ are zero (if Z_1



Realization of Low Pass Function

- Transmission zeros are when series impedance becomes infinite.


$$sL \rightarrow \infty \Rightarrow s \rightarrow \infty \Rightarrow \frac{1}{sC + 1/R} \rightarrow 0$$

$$T(s) = \frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2} = \frac{Y_1}{Y_1 + Y_2} = \frac{1/sL}{1/sL + sC + 1/R}$$

High Pass Filter

- Use the series capacitor.
Transmission zero at $s=0$ (dc), shunt inductor is a transmission zero at $s=0$.

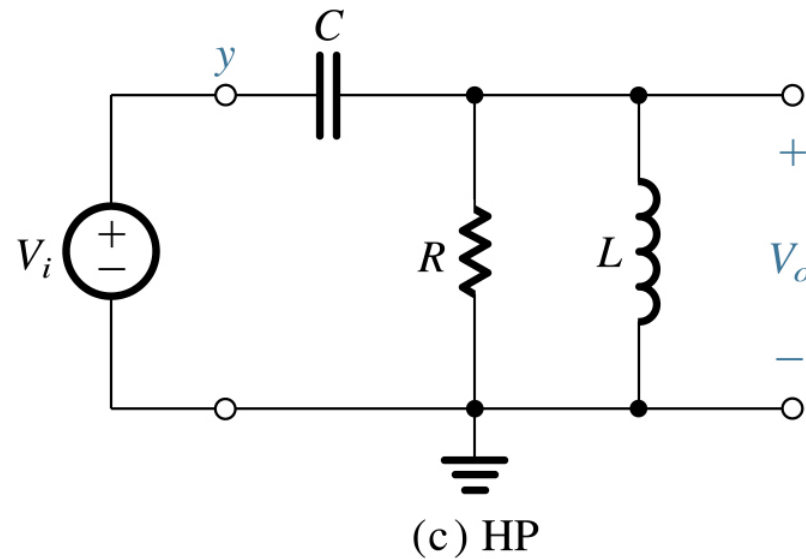
$$T(s) = \frac{V_o}{V_i} = \frac{a_2 s^2}{s^2 + s(\omega_0 / Q) + \omega_0^2}$$



Bandpass Filter



- Zero at $s=0$ due to shunt inductor, $s=\infty$ due to shunt capacitor.
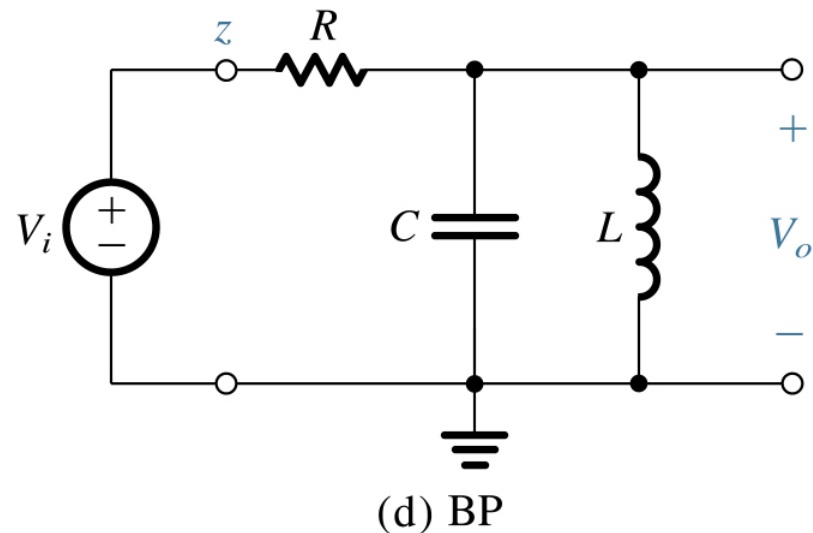
$$T(s) = \frac{V_o}{V_i} = \frac{s(1/CR)}{s^2 + s(1/CR) + 1/LC}$$





Inductance Simulation

- Use opamps instead of inductor!

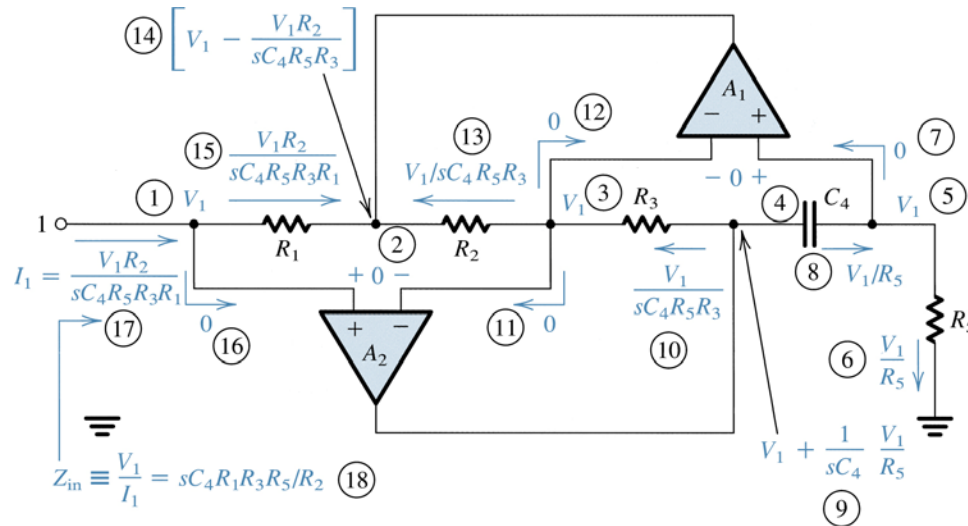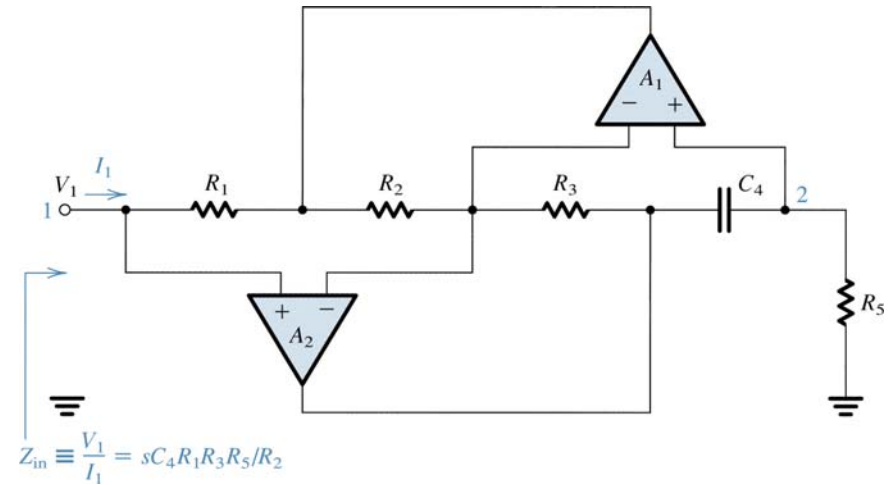

Low Pass Filter

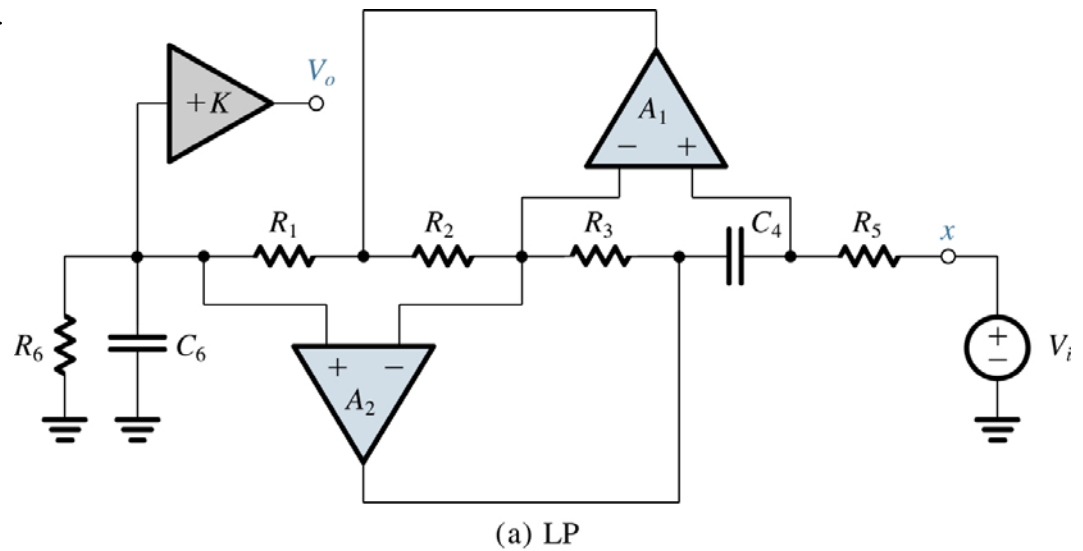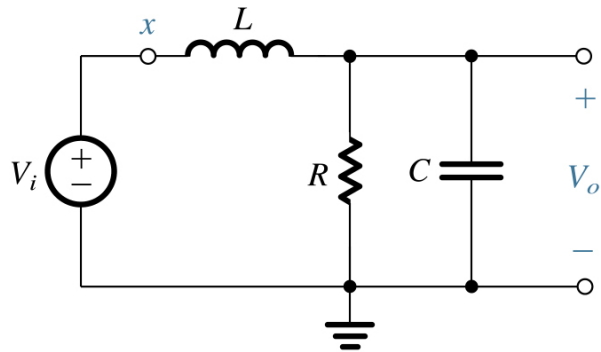
$$T(s) = \frac{V_o(s)}{V_i(s)} = \frac{Z_2(s)}{Z_1(s) + Z_2(s)}$$




$$T(s) = \frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2} = \frac{Y_1}{Y_1 + Y_2} = \frac{1/sL}{1/sL + sC + 1/R}$$

High Pass Filter

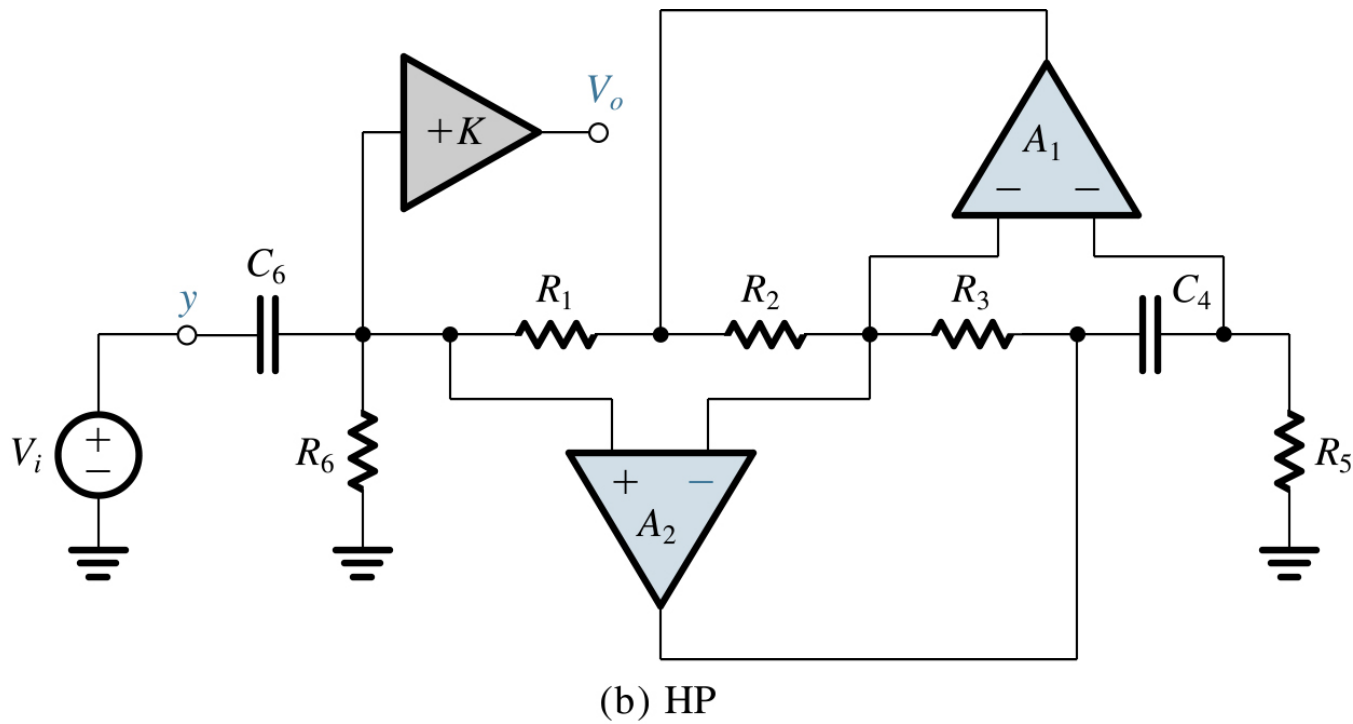- $$T(s) = \frac{V_o}{V_i} = \frac{a_2 s^2}{s^2 + s(\omega_0 / Q) + \omega_0^2}$$




Bandpass Filter

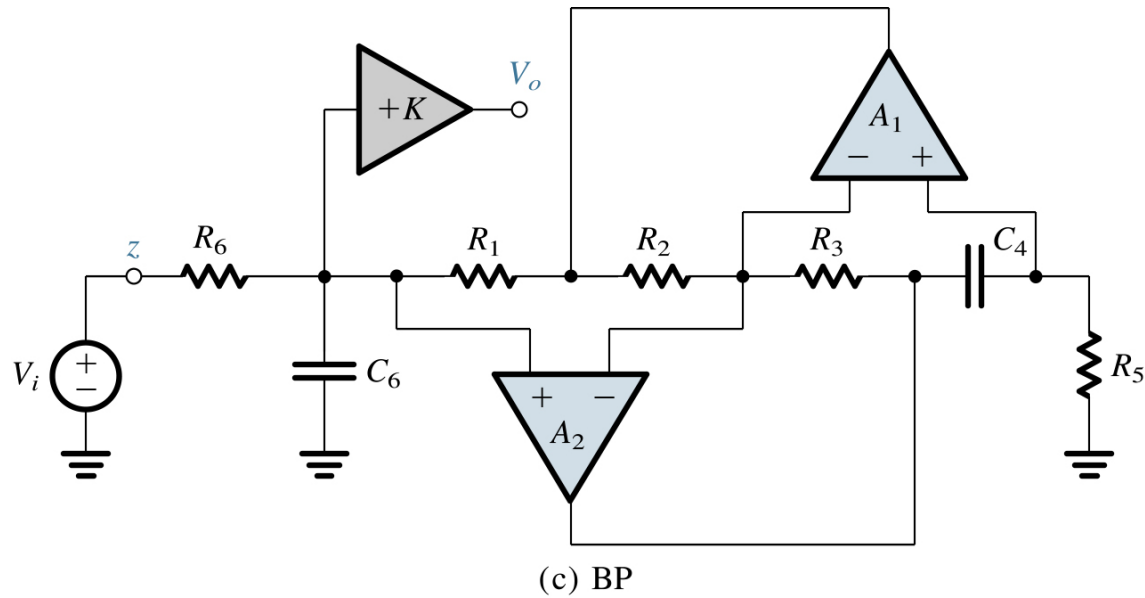

$$T(s) = \frac{V_o}{V_i} = \frac{s(1/CR)}{s^2 + s(1/CR) + 1/LC}$$


Low Pass Notch filter

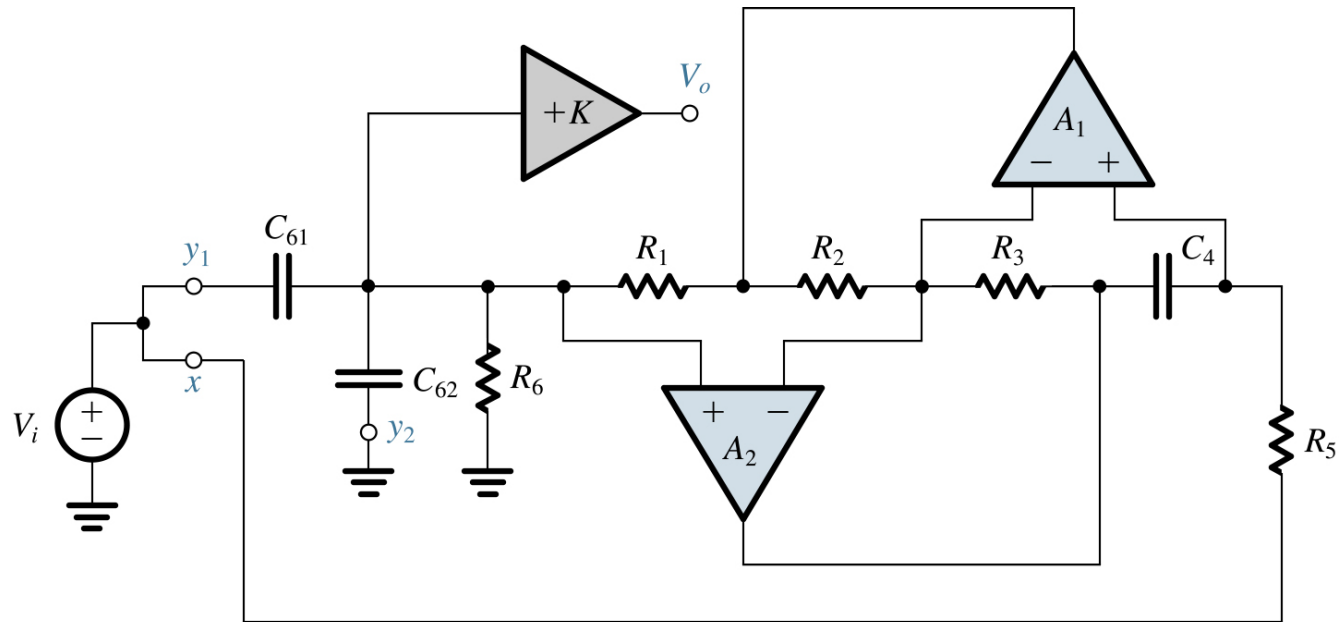

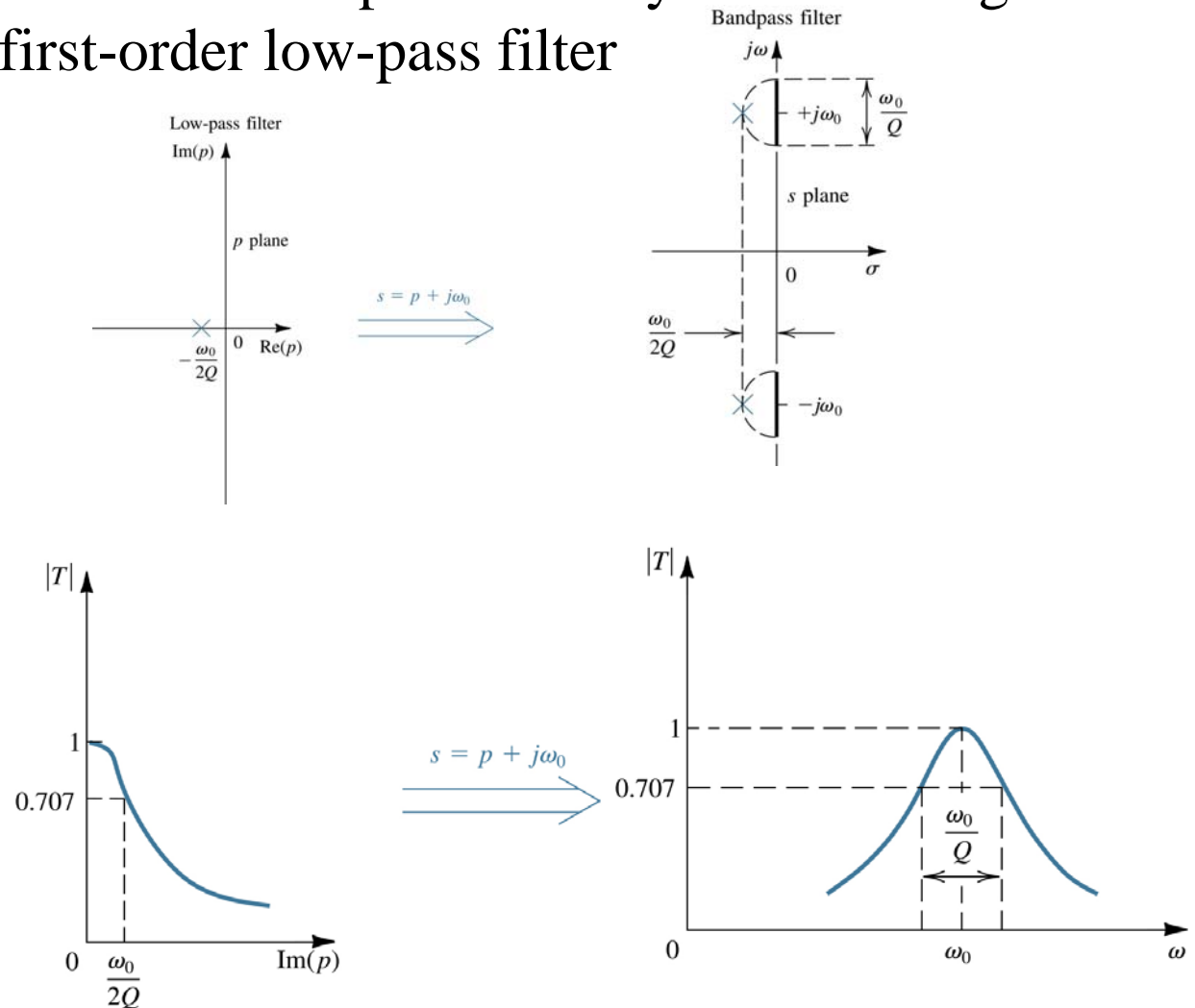
(e) LPN, $\omega_n \geq \omega_0$

Second-order narrow-band bandpass filter by transforming a first-order low-pass filter

Second-order narrow-band bandpass filter by transforming a first-order low-pass filter. **(a)** Pole of the first-order filter in the s -plane. **(b)** Applying the transformation $s = p + j\omega_0$ and adding a complex conjugate pole results in the poles of the second-order bandpass filter. **(c)** Magnitude response of the first-order low-pass filter. **(d)** Magnitude response of the second-order bandpass filter.




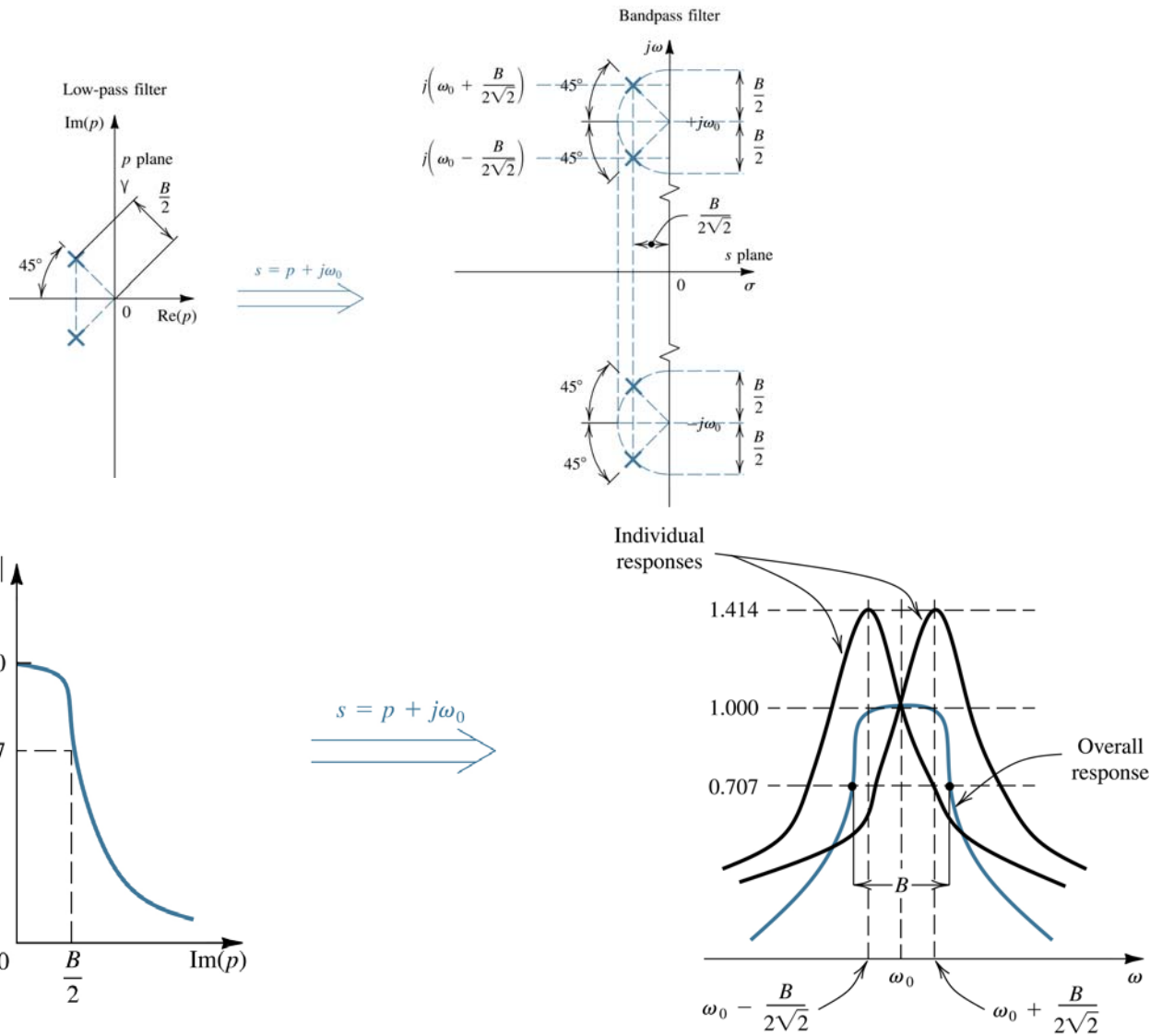Poles and the frequency response of a fourth-order stagger-tuned narrow-band bandpass amplifier by transforming a second-order low-pass .




SIGNAL GENERATORS /OSCILLATORS

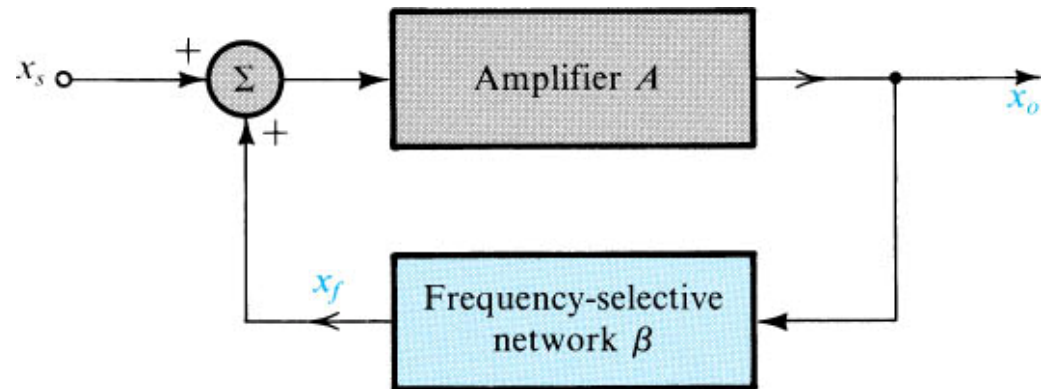A positive-feedback loop is formed by an amplifier and a frequency-selective network




In an actual oscillator circuit, no input signal will be present


Oscillator-frequency stability

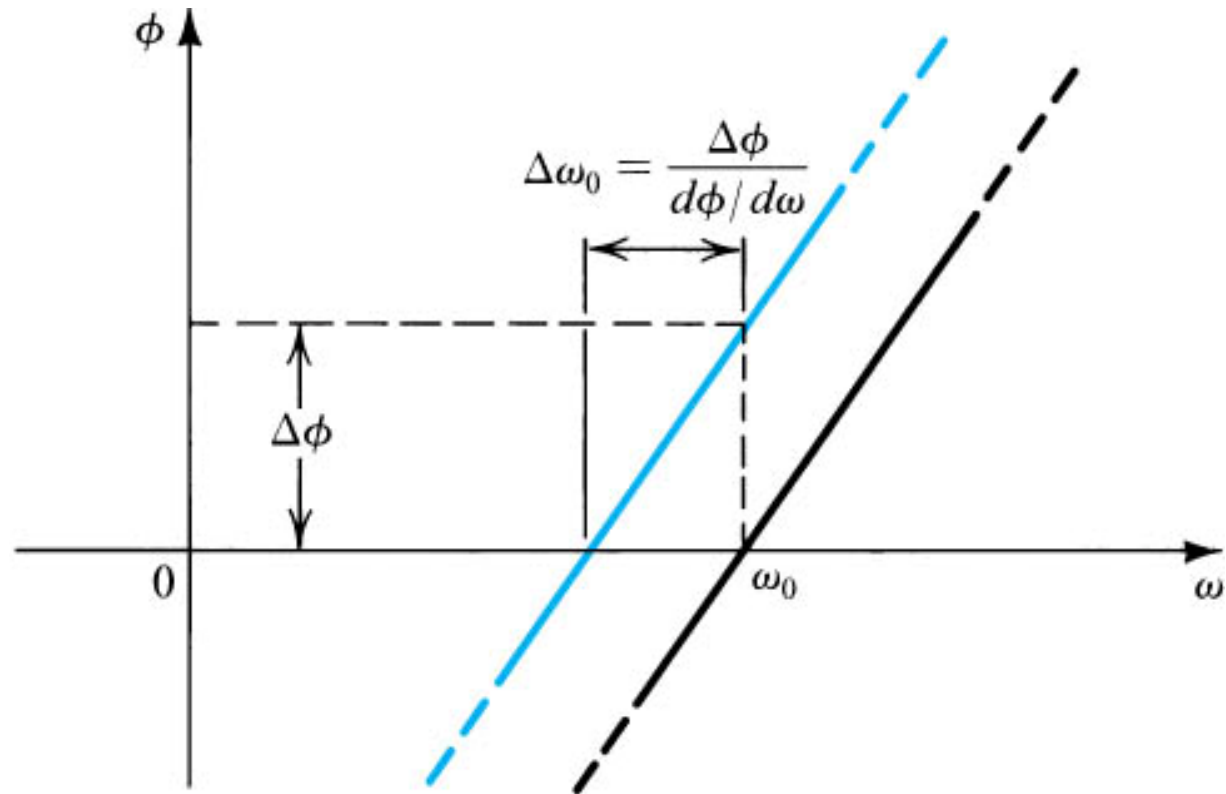


Limiter Ckt \rightarrow Comparator

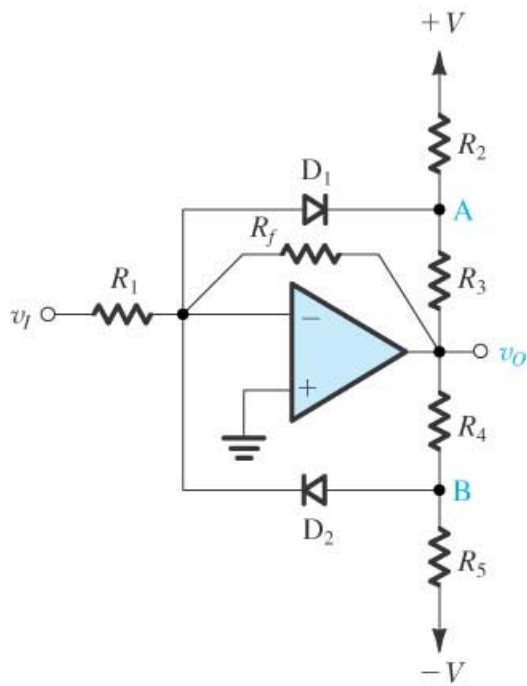

(a)

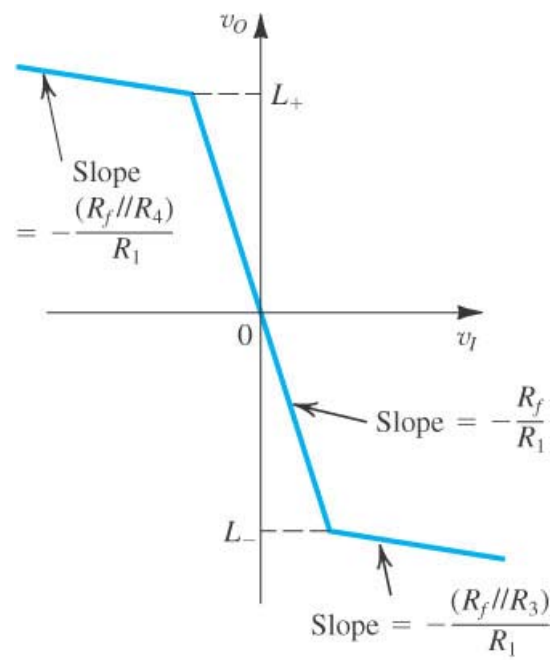


(b)

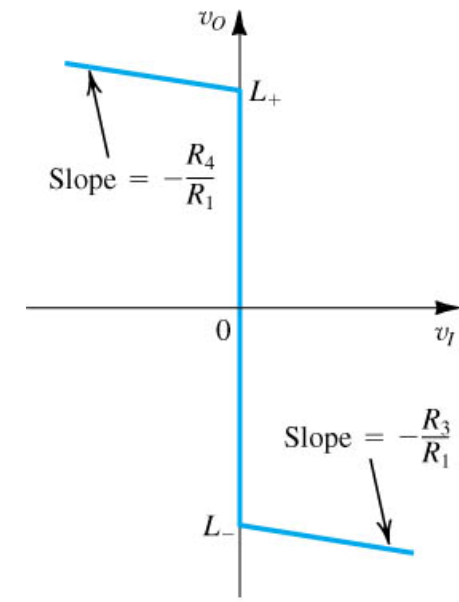

(c)


Wien-bridge oscillator

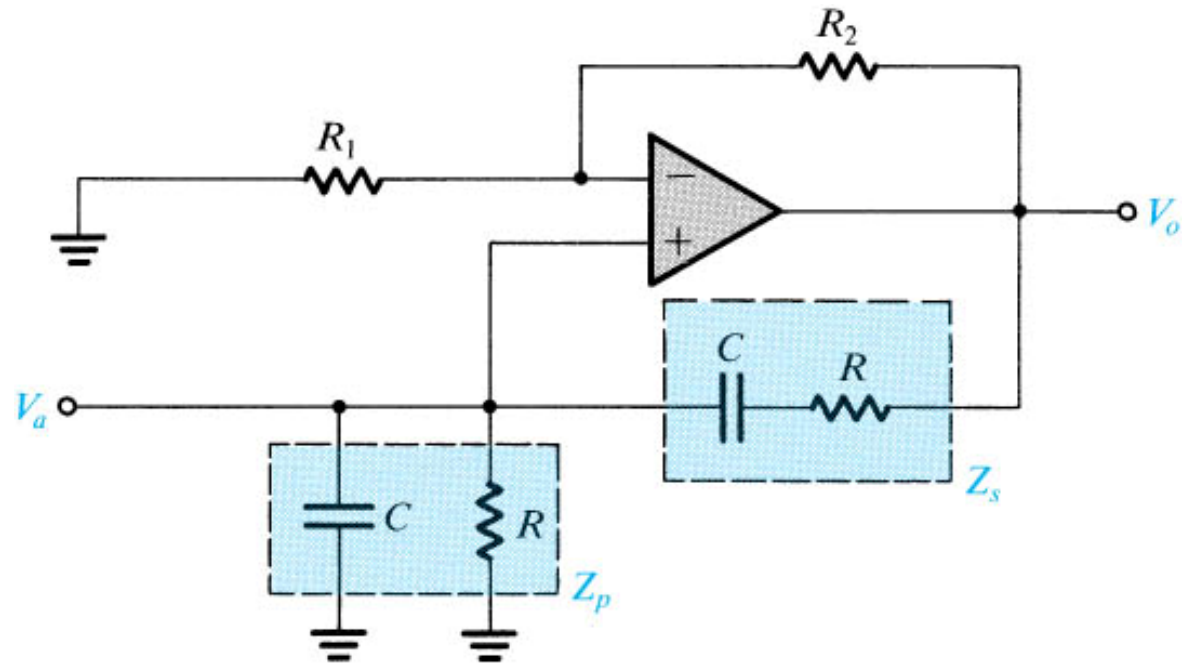


without amplitude
stabilization.

Wien bridge w/ Amp. Stabil.


limiter used for amplitude control.

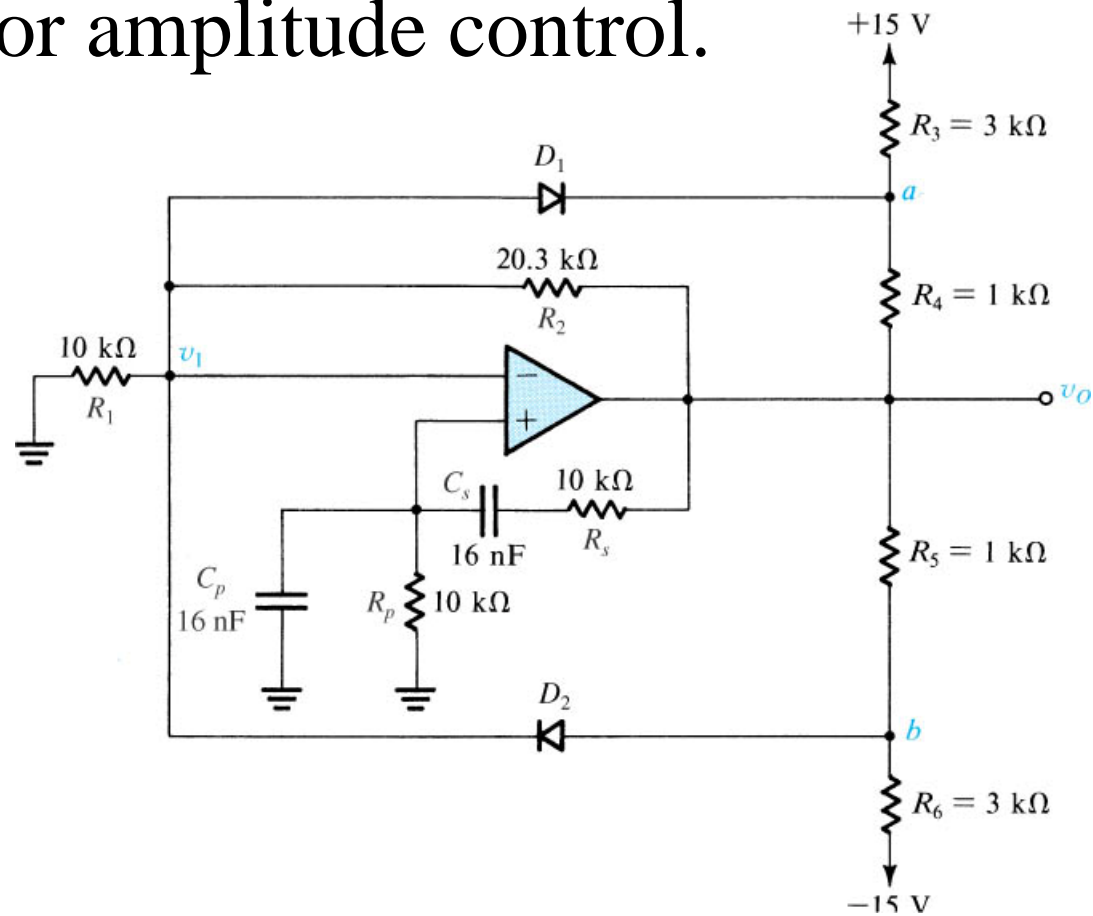


Alternate Wien bridge stabil.

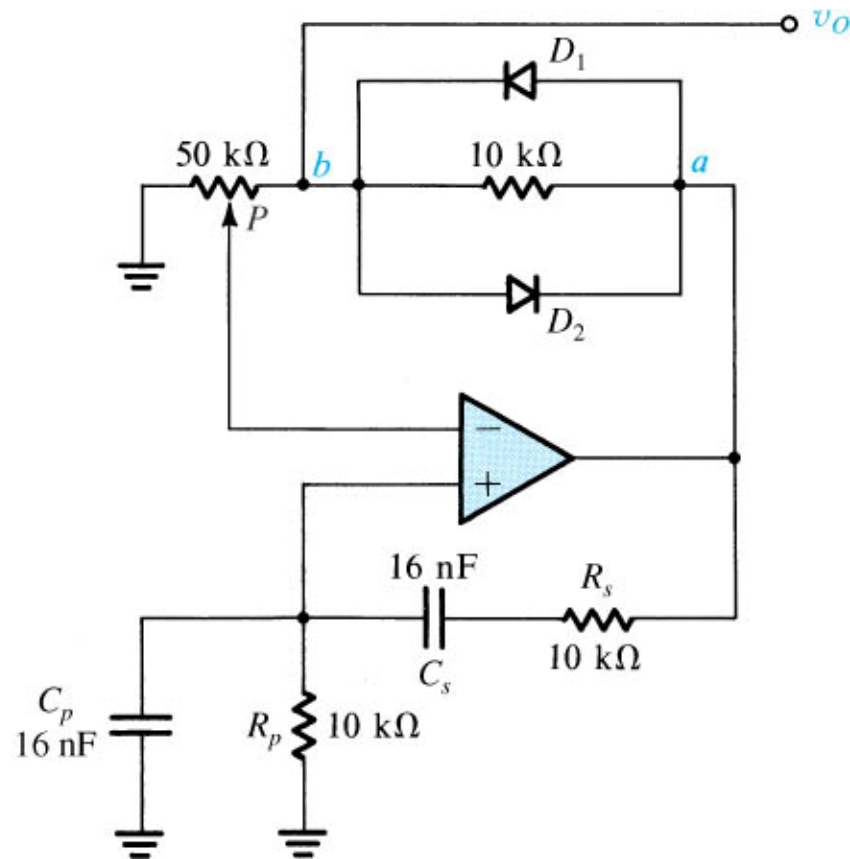


Phase Shift Oscillator

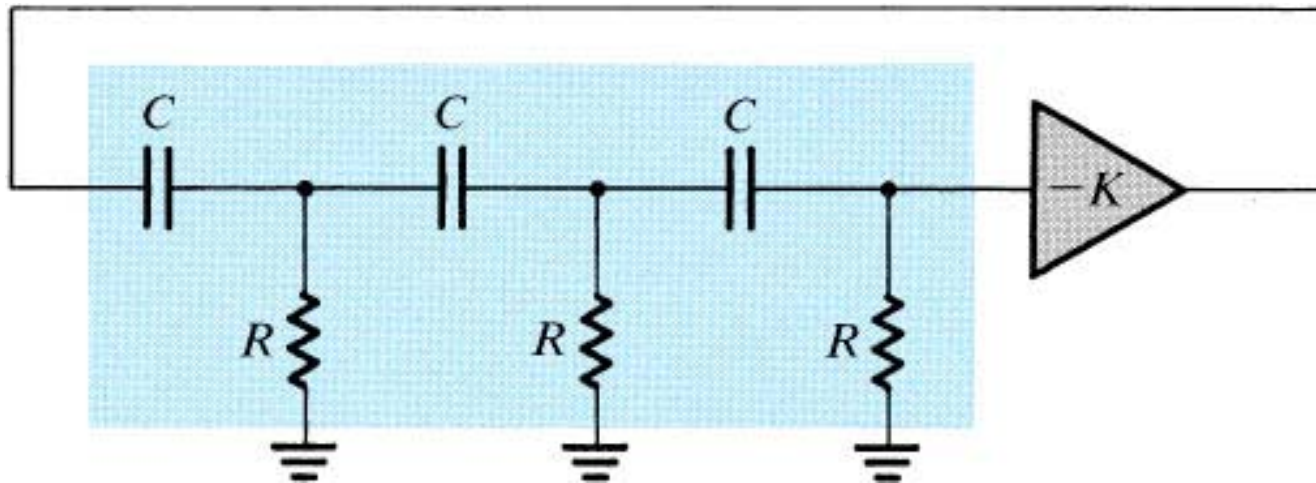


Phase Shift. Osc. W/ Stabil.

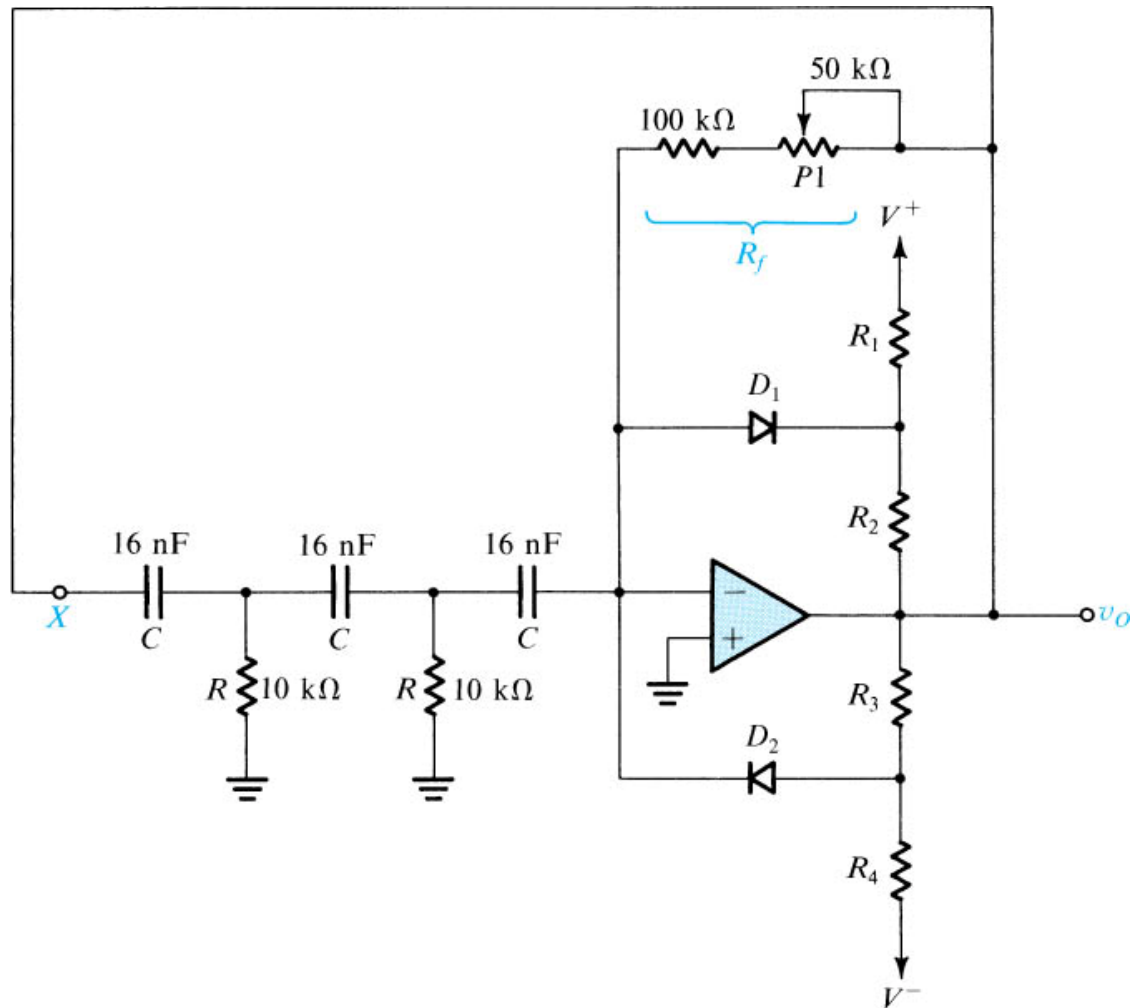

Quad Osc. Circuit

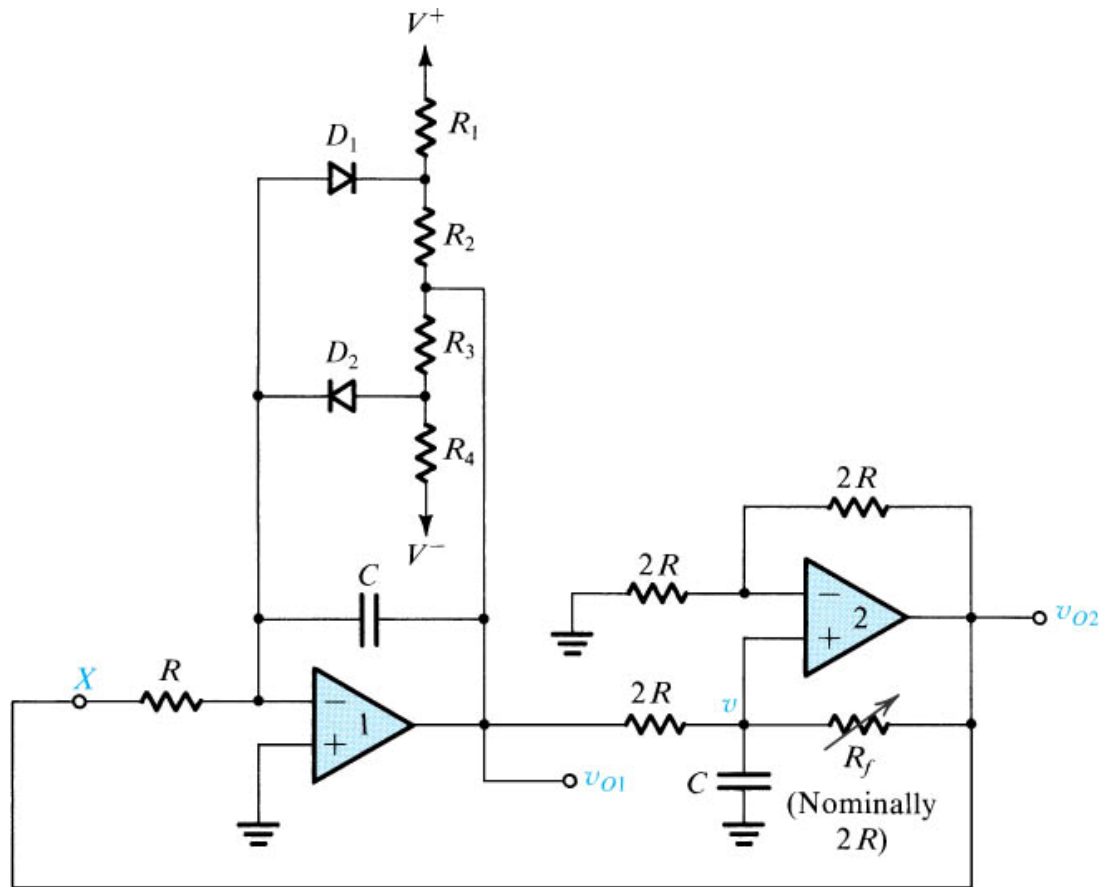


(a)

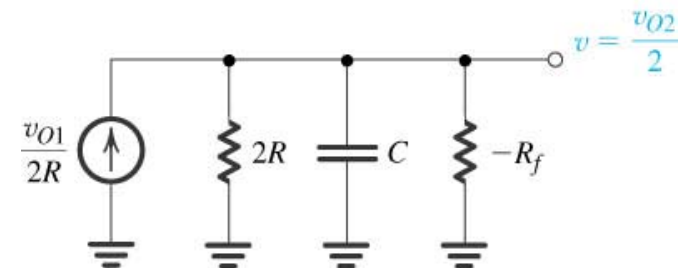


(b)


Active Tuned Osc.

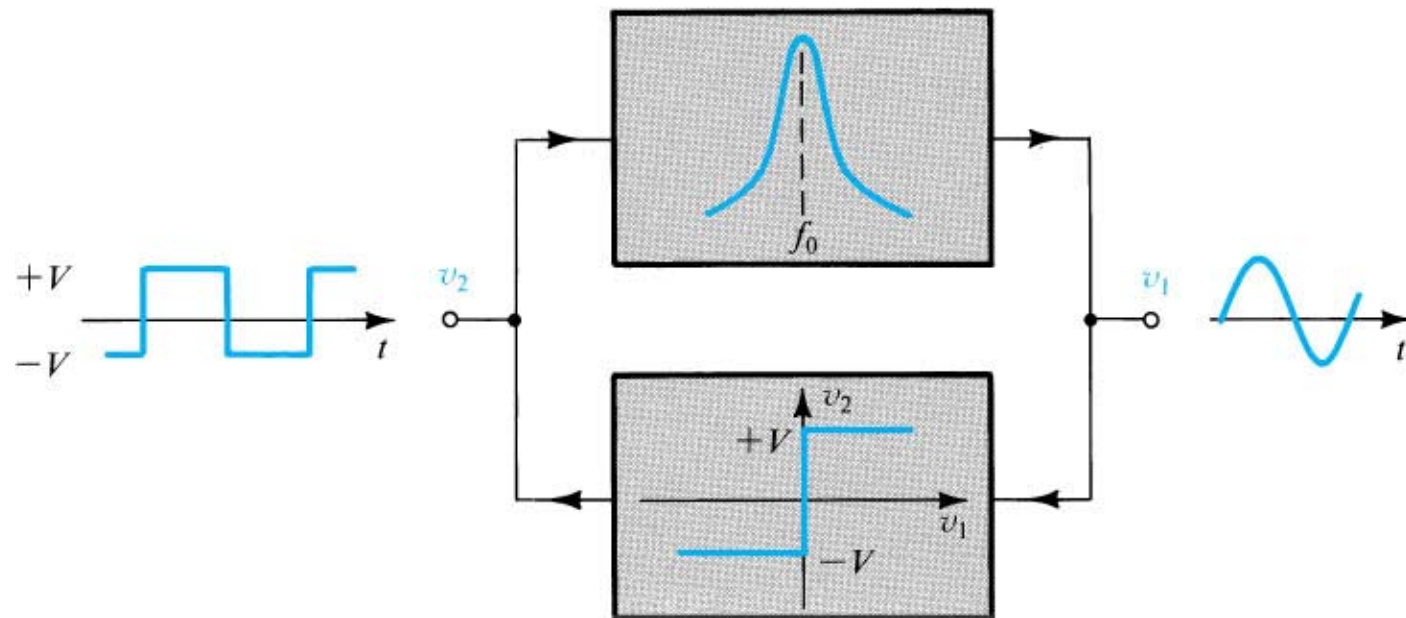

Colpitts and Hartley Oscillators

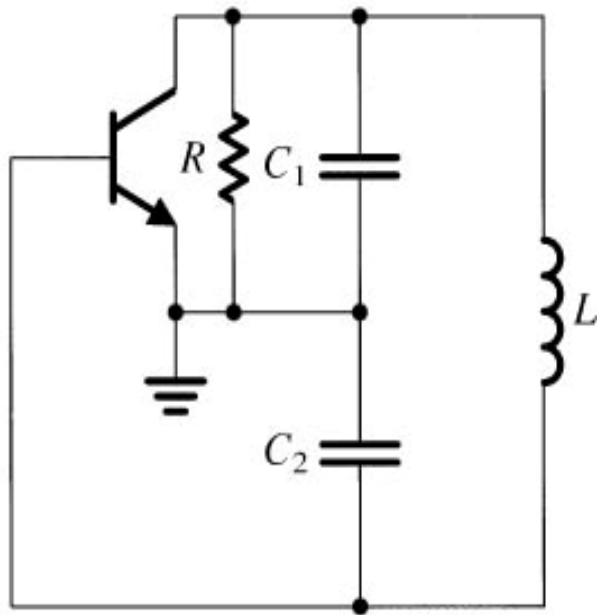

(a)

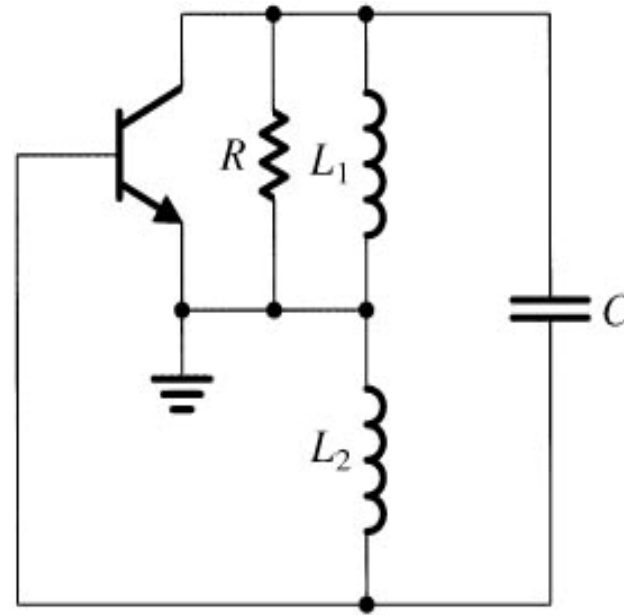


(b)


Equiv. Ckt

To simplify the analysis, neglect C_m and r_p

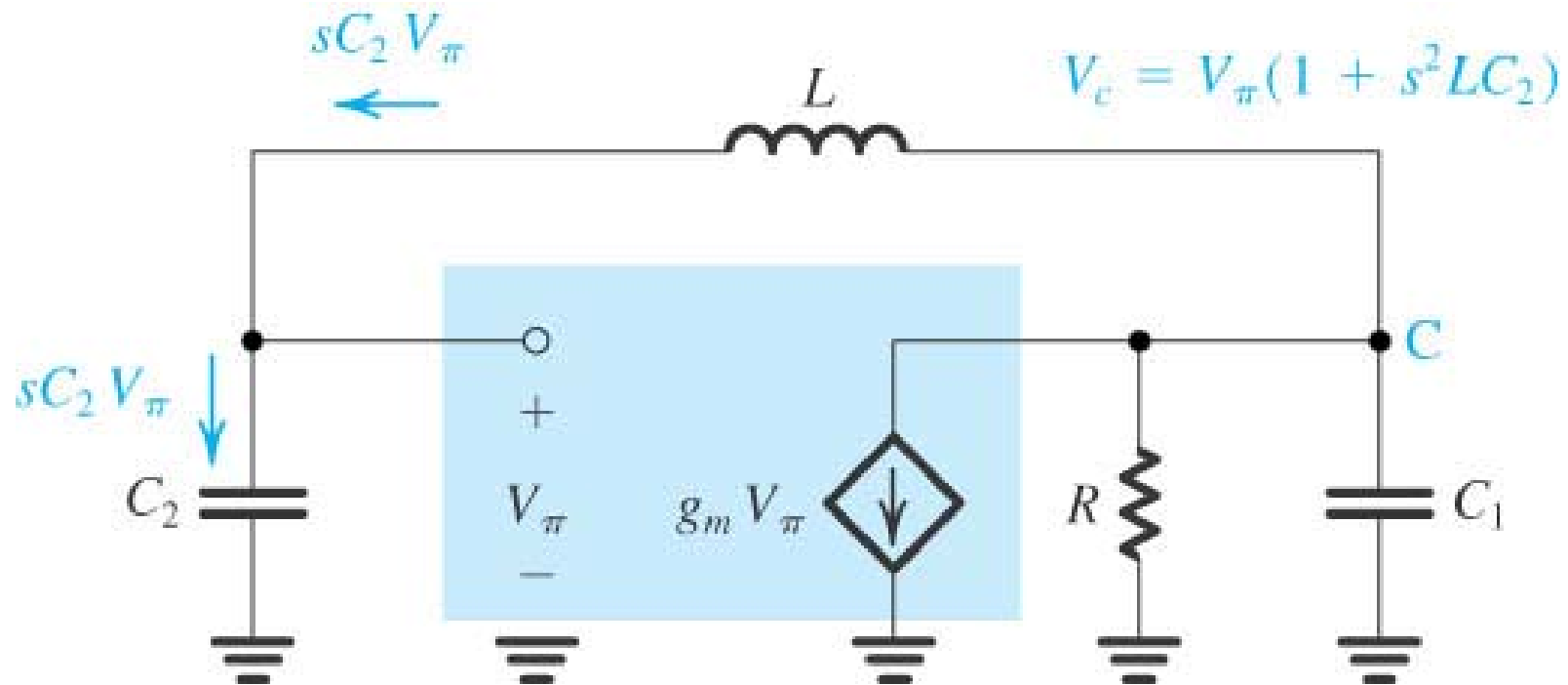Consider C_p to be part of C_2 , and include r_o in R .




Collpits Oscillator

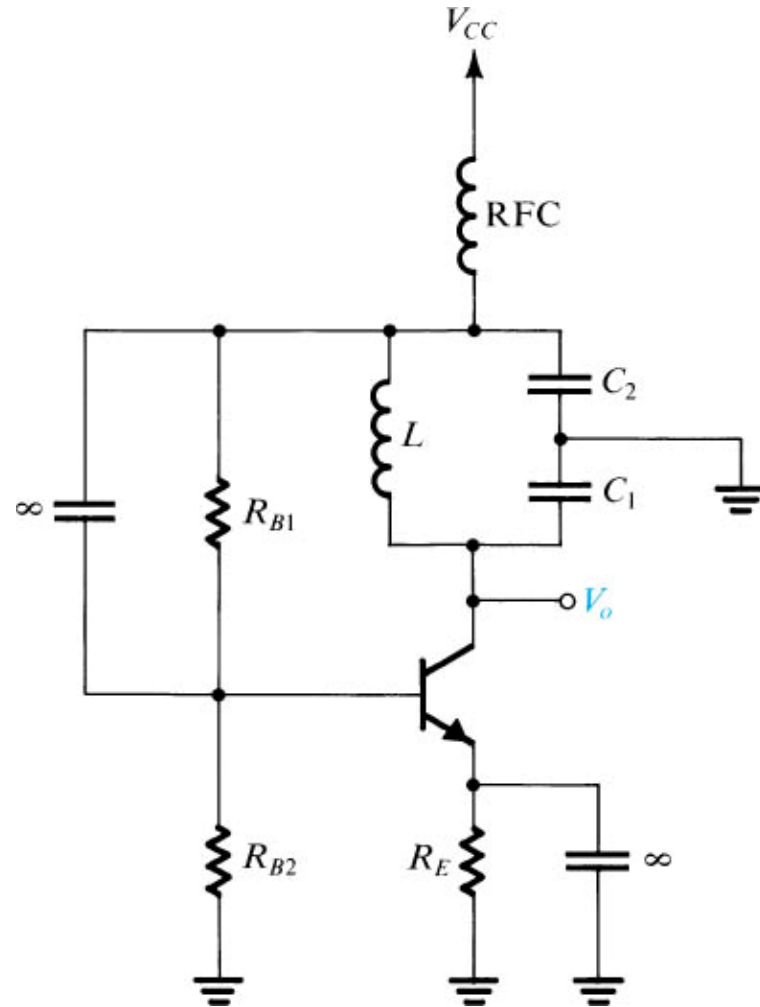


Piezoelectric Crystal



(a)

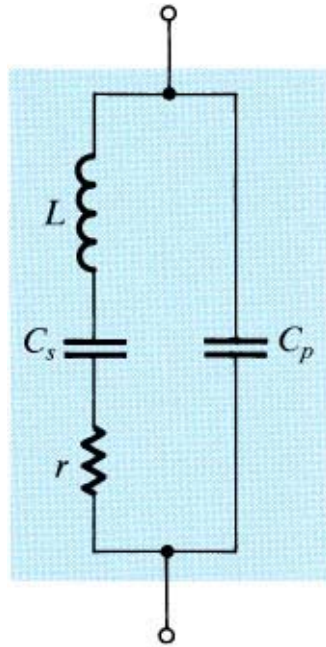


(b)

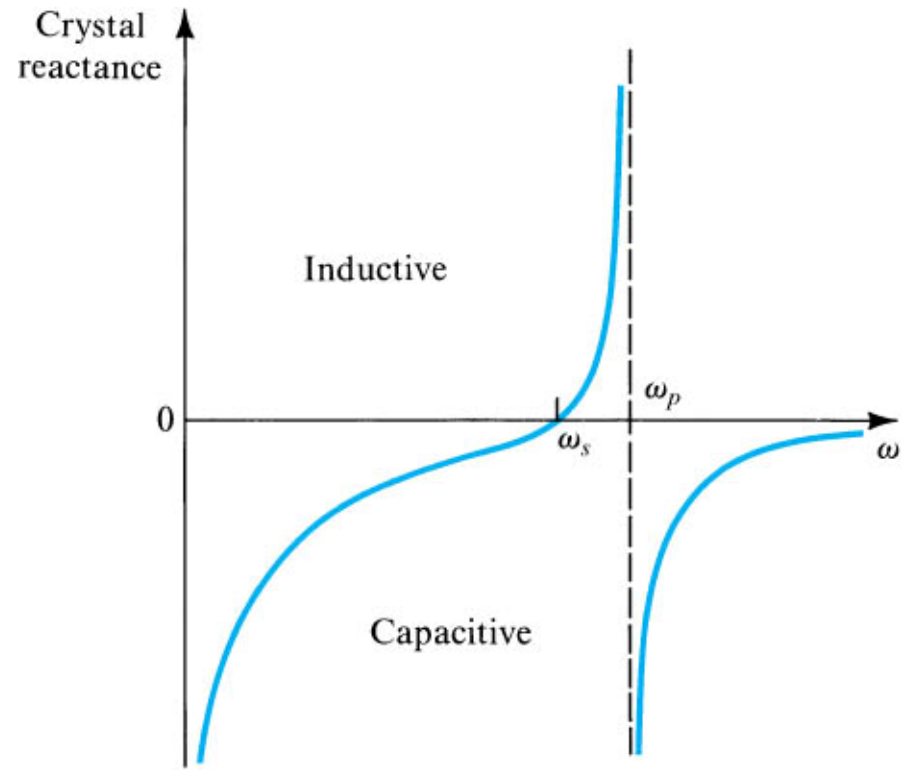

(c)

Pierce Oscillator

CMOS inverter as an amplifier.

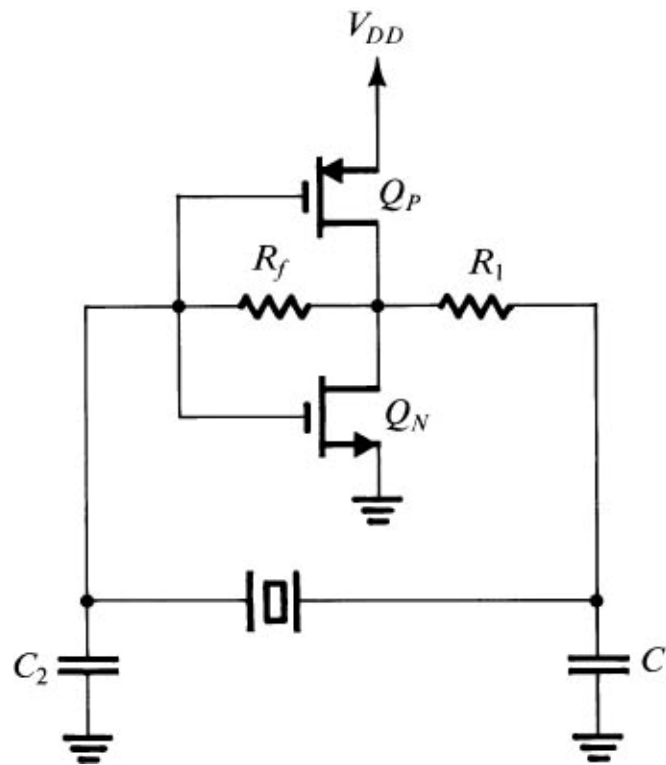

Bistable Operation

